

# Lecture 24

## Multistage Amplifiers (I)

### MULTISTAGE AMPLIFIER

### Outline

1. Introduction
2. CMOS multi-stage voltage amplifier
3. BiCMOS multistage voltage amplifier
4. BiCMOS current buffer
5. Coupling amplifier stages

#### **Reading Assignment:**


Howe and Sodini, Chapter 9, Sections 9-1-9.3

# 1. Introduction

Most often, single stage amplifier does not accomplish design goals:

- Need more gain than could be provided by a single stage
- Need to adapt to specified  $R_S$  and  $R_L$  to maximize efficiency

⇒ *Multistage amplifier*

 

Issues:

- What amplifying stages should be used and in what order?
- What devices should be used, BJT or MOSFET?
- How is biasing to be done?

## Summary of single stage amplifier characteristics

Stage	$A_{vo}, A_{io}$	$R_{in}$	$R_{out}$	Key Function
<b>Common Source</b>	$A_{vo} = -g_m(r_o // r_{oc})$	$\infty$	$r_o // r_{oc}$	Transconductance amplifier
<b>Common Drain</b>	$A_{vo} \approx \frac{g_m}{g_m + g_{mb}}$	$\infty$	$\frac{1}{g_m + g_{mb}}$	Voltage Buffer
<b>Common Gate</b>	$A_{io} \approx -1$	$\frac{1}{g_m + g_{mb}}$	$r_{oc} // [r_o(1 + g_m R_S)]$	Current buffer
<b>Common Emitter</b>	$A_{vo} = -g_m(r_o // r_{oc})$	$r_\pi$	$r_o // r_{oc}$	Transconductance amplifier
<b>Common Collector</b>	$A_{vo} \approx 1$	$r_\pi + \beta_o(r_o // r_{oc} // R_L)$	$\frac{1}{g_m} + \frac{R_S}{\beta_o}$	Voltage buffer
<b>Common Base</b>	$A_{io} \approx -1$	$\frac{1}{g_m}$	$r_{oc} // [r_o(1 + g_m(r_\pi // R_S))]$	Current buffer

### Differences between BJT's and MOSFETs

**BJT**

**MOSFET**

$$r_\pi = \frac{\beta_o}{g_m}$$

$$g_{mb} \propto g_m$$

$$g_m = \frac{I_C}{V_{th}}$$

$$g_m = \sqrt{2 \frac{W}{L} \mu C_{ox} I_D}$$

$$r_o = \frac{V_A}{I_C}$$


$$r_o = \frac{1}{\lambda I_D}$$

## 2. CMOS Multistage Voltage Amplifier

Goals:

- High voltage gain,  $A_{vo}$
- High input resistance,  $R_{in}$
- Low output resistance,  $R_{out}$

 
Good starting point: Common-Source stage:



- $R_{in} = \infty$
- $A_{vo} = -g_m(r_o//r_{oc})$ , probably insufficient
- $R_{out} = (r_o//r_{oc})$ , too high


## CMOS Multistage Voltage Amplifier (contd.)

Add second CS stage to get more gain:

 

- $R_{in} = \infty$
- $A_{vo} = g_{m1}(r_{o1} \parallel r_{oc1}) g_{m2}(r_{o2} \parallel r_{oc2})$
- $R_{out} = (r_{o2} \parallel r_{oc2})$ , still too high

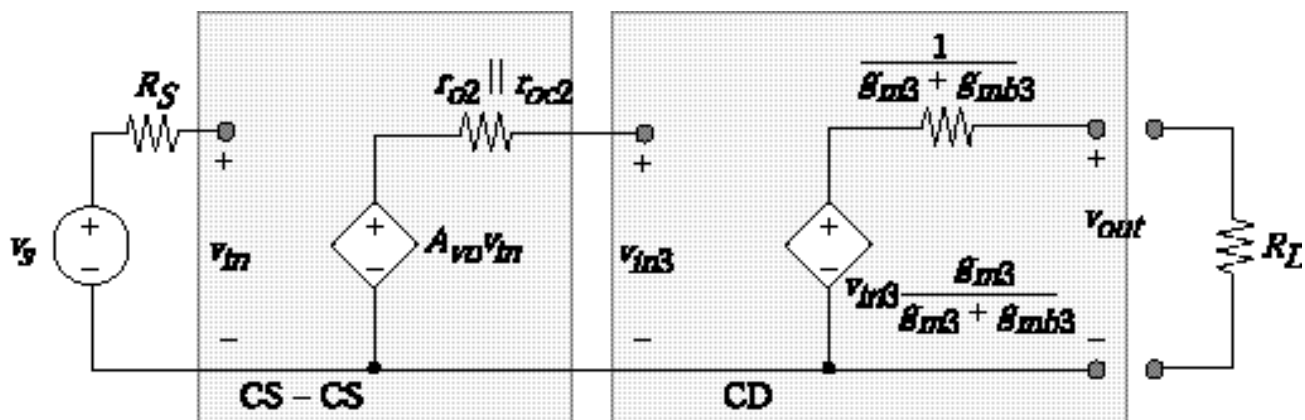Add CD stage at output (to reduce  $R_{out}$ ):




- $R_{in} = \infty$
- $A_{vo} = g_{m1}(r_{o1} \parallel r_{oc1}) g_{m2}(r_{o2} \parallel r_{oc2}) \frac{g_{m3}}{g_{m3} + g_{mb3}}$
- $R_{out} = \frac{1}{g_{m3} + g_{mb3}}$

### 3. BiCMOS multistage voltage amplifier

$A_{vo}(CE) > A_{vo}(CS)$  because  $r_o(\text{BJT}) > r_o(\text{MOSFET})$ , but..

CS stage is best first stage, since  $R_{in} = \infty$ .

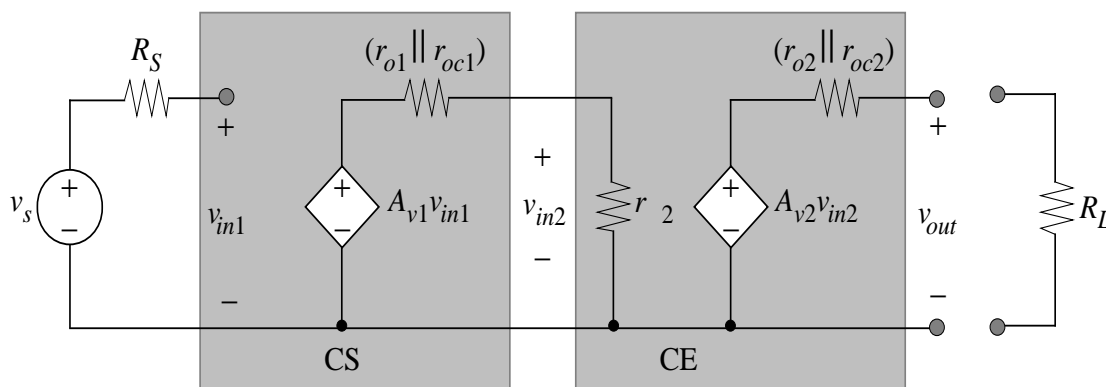How about adding a CE stage following the CS stage?



However, inter-stage loading degrades gain:

$$R_{out1} = r_{o1} \parallel r_{oc1} \gg R_{in2} = r_{\pi 2}$$


There is a voltage divider between stages

$$\frac{R_{in2}}{R_{out1} + R_{in2}} \approx \frac{R_{in2}}{R_{out1}} \approx \frac{r_{\pi 2}}{r_{o1} \parallel r_{oc1}} \ll 1$$

Additional gain provided by the CE stage is mostly lost to inter-stage loading.
 
## BiCMOS multistage voltage amplifier (contd.)

Use two CS stages, but add CC stage at output:



Inter-stage loading:

$$R_{out2} = r_{o2} \parallel r_{oc2}, \quad R_{in3} = r_{\pi3} + \beta_{o3} (r_{o3} \parallel r_{oc3} \parallel R_L)$$

Then, inter-stage loss:

$$\frac{R_{in3}}{R_{out2} + R_{in3}} = \frac{r_{\pi3} + \beta_{o3} (r_{o3} \parallel r_{oc3} \parallel R_L)}{r_{o2} \parallel r_{oc2} + r_{\pi3} + \beta_{o3} (r_{o3} \parallel r_{oc3} \parallel R_L)}$$

Better than trying to use a CE stage, but still pretty bad.

The good thing is that  $R_{out}$  has improved:

$$R_{out} = R_{out3} = \frac{1}{g_{m3}} + \frac{R_{out2}}{\beta_{o3}} = \frac{1}{g_{m3}} + \frac{r_{o2} \parallel r_{oc2}}{\beta_{o3}}$$

Since, in general  $g_m(\text{BJT}) > g_m(\text{MOSFET})$ ,  $R_{out}$  could be better than CD output stage if  $r_{o2} \parallel r_{oc2}$  is not too large.


Otherwise, CD output stage is better.

# BiCMOS multistage voltage amplifier (contd.)

Better voltage buffer: cascade CC and CD output stages

What is the best order?

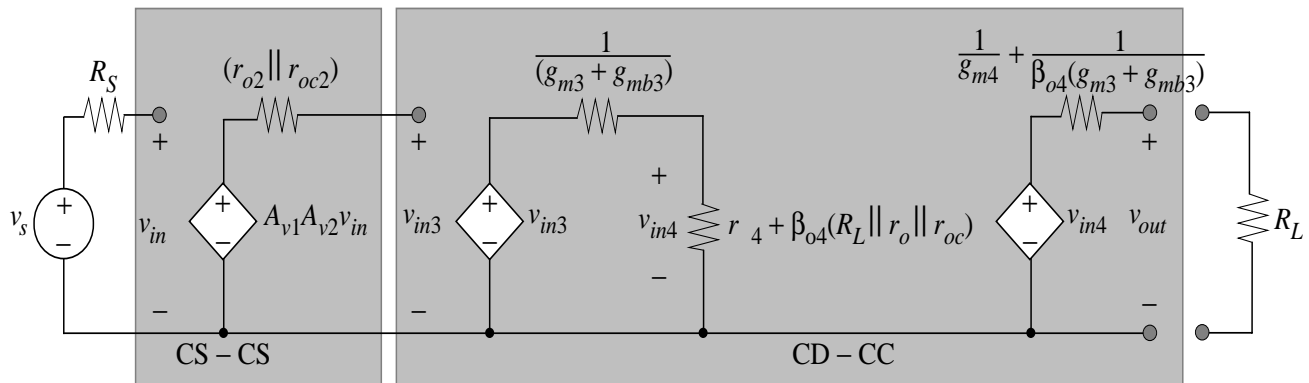Since  $R_{in}(CD) = \infty$ , best to place CD first:



Inter-stage loading:

$$\frac{R_{in3}}{R_{in3} + R_{out2}} = 1$$

$$\frac{R_{in4}}{R_{in4} + R_{out3}} = \frac{r_{\pi4} + \beta_{o4}(r_{o4} \parallel r_{oc4} \parallel R_L)}{\frac{1}{g_{m3} + g_{mb3}} + r_{\pi4} + \beta_{o4}(r_{o4} \parallel r_{oc4} \parallel R_L)} \approx 1$$

The output resistance is excellent:

$$R_{out} = R_{out4} = \frac{1}{g_{m4}} + \frac{R_{out3}}{\beta_{o4}} = \frac{1}{g_{m4}} + \frac{1}{\beta_{o4}(g_{m3} + g_{mb3})}$$




## 4. BiCMOS current buffer

### Goals:

- Unity current gain,  $A_i=1$
- Very low input resistance,  $R_{in}$
- Very high output resistance,  $R_{out}$

Start with a common-base stage:

 


- $A_{io} = -1$
- $R_{in} = \frac{1}{g_m}$
- $R_{out} = r_{oc} \parallel \left\{ r_o \left[ 1 + g_m (r_\pi \parallel R_S) \right] \right\}$

Note that if  $R_S$  is “high enough”,  $R_{out} \approx r_{oc} \parallel (\beta_o r_o)$ .

Can we increase  $R_{out}$  further by adding a second CB stage?

# BiCMOS current buffer (contd).

## CB-CB Current Buffer

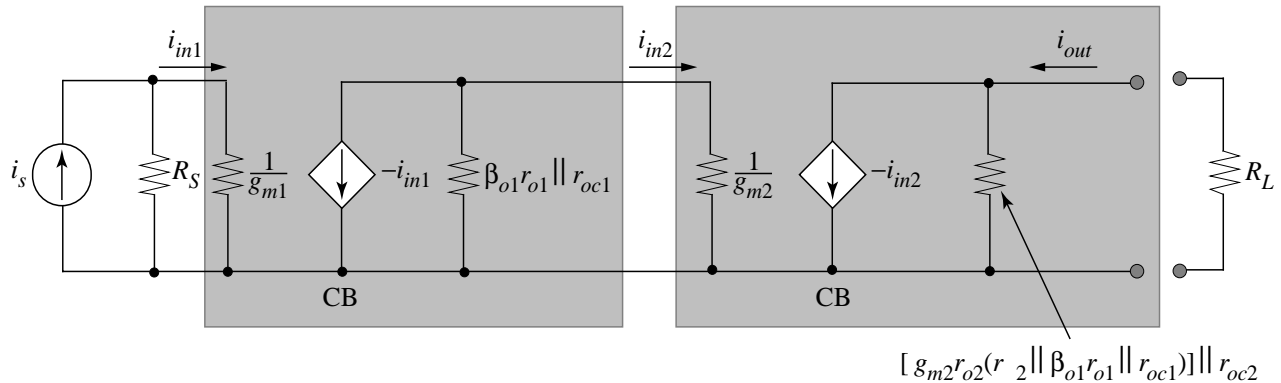

Now

$$R_{out} = R_{out2} = r_{oc2} \parallel \left\{ r_{o2} \left[ 1 + g_{m2} (r_{\pi2} \parallel R_{out1}) \right] \right\}$$

Plugging in  $R_{out1} \approx r_{oc1} \parallel (\beta_{o1} r_{oc1})$ .

$$R_{out} = r_{oc2} \parallel \left\{ r_{o2} \left[ 1 + g_{m2} (r_{\pi2} \parallel r_{oc1} \parallel \beta_{o1} r_{oc1}) \right] \right\}$$

But, since  $r_{\pi2} \ll r_{oc1} \parallel (\beta_{o1} r_{oc1})$ , then


$$R_{out} = r_{oc2} \parallel \left[ r_{o2} (1 + g_{m2} r_{\pi2}) \right] \approx r_{oc2} \parallel (\beta_{o2} r_{o2})$$

**Did not improve anything!** The base current limits the number of CB stages that can improve the output resistance to just one.

Since the CG stage has no gate current, cascade it with the CB stage

## BiCMOS current buffer (contd).

### CB-CG Current Buffer

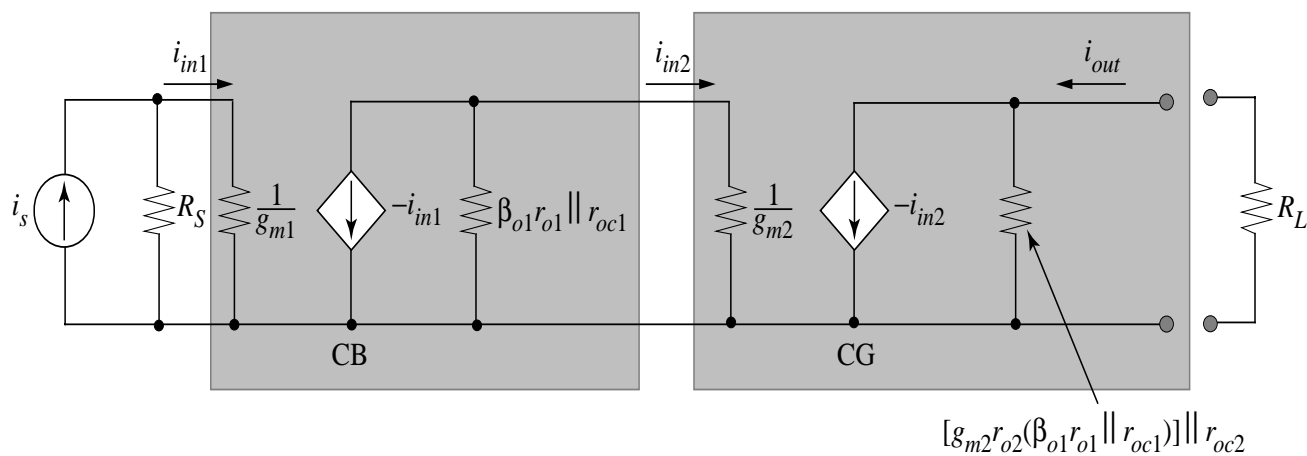

$$R_{out} = R_{out2} = r_{oc2} \parallel [r_{o2} (1 + g_{m2} R_{out1})]$$

Plugging in  $R_{out1} \approx r_{oc1} \parallel (\beta_{o1} r_{o1})$ .

$$R_{out} = r_{oc2} \parallel [r_{o2} g_{m2} (r_{oc1} \parallel \beta_{o1} r_{o1})]$$


Now  $R_{out}$  has improved by about  $g_{m2} r_{o2}$ , but only to the extent that  $r_{oc2}$  is high enough...

## 5. Coupling Amplifier Stages

### CAPACITIVE COUPLING

Capacitors that have large enough value behave as AC short, so the signal goes through but bias is independent for each stage.

Example, CD-CC voltage buffer:

 


- Advantages
  - Can select bias point for optimum operation
  - Can select bias point close to the mid-point of the power rails for maximum voltage swing
- Disadvantages
  - To approximate AC short, large capacitors are needed and they consume large area.

## Coupling Amplifier Stages (contd.)

**DIRECT COUPLING: share bias points across stages.**

Example, CD-CC voltage buffer:

 


Assumes  $V_{BE} = 0.7 \text{ V}$

$V_{GS} = 1.5 \text{ V}$

- Advantages
  - No capacitors needed
  - compact
- Disadvantages
  - Bias point shared:constrains designs.
  - Bias shifts from stage to stage and can stray too far from center of range
  - Generally requires level shifting to bring signal back to center of range.
 
# Coupling Amplifier Stages (contd.)

**SOLUTION:** use PMOS CD stage for level shifting.



Assumes  $V_{BE} = 0.7 \text{ V}$

$V_{GS} = 1.5 \text{ V}$

# Coupling Amplifier Stages (contd.)

Summary of DC shifts through amplifier stages:

Amplifier Type	Transistor Type			
	NMOS	PMOS	nnp	pnp
Common Source/ Common Emitter (CS/CE)				
Common Gate/ Common Base (CG/CB)				
Common Drain/ Common Collector (CD/CC)				

# What did we learn today?

## Summary of Key Concepts

- To achieve design goals, multistage amplifiers are often needed
- In multistage amplifiers, different stages are used to accomplish different goals
  - **Voltage gain**: common-source, common emitter
  - **Voltage buffer**: common drain, common collector
  - **Current buffer**: common gate, common base
- In multistage amplifiers, attention must be paid to inter-stage loading to avoid unnecessary losses
  - Must select compromise bias,
  - Must pay attention to bias shift from stage to stage