

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.012 Microelectronic Devices and Circuits  
Spring 2007

Homework #7 – Due May 4, 2007

Problem 1:

- a.) To obtain  $V_{OUT}=0V$ , we need  $I_{OUT}=0A$ , so  $I_C$  must equal  $I_{SUP}$ . Using this information, we can calculate  $V_{BE}$  as well as the voltage drop across  $R_S$ . Adding these drops to the negative voltage supply yields the necessary  $V_{BIAS}$ .

$$V_{BE} = V_{th} \ln\left(\frac{I_C}{I_S}\right) = 0.025 \cdot \ln\left(\frac{100\mu A}{1fA}\right) = 633mV$$

$$I_B R_S = \frac{I_C}{\beta} R_S = \left(\frac{100\mu A}{100}\right) \cdot 1k\Omega = 1mV$$

$$V_{BIAS} = V_{BE} + I_B R_S - 2.5V = -1.866V$$

- b.) The input resistance for a common-emitter equals  $r_\pi$ .

$$R_{in} = \frac{\beta V_{th}}{I_C} = \frac{100 \cdot 0.025V}{100\mu A} = 25k\Omega$$


- c.) The unloaded voltage gain  $A_{vo}$  for a common-emitter equals  $-g_m r_o$ .

$$A_{vo} = -g_m r_o = \frac{-I_C}{V_{th}} \cdot \frac{V_A}{I_C} = -\frac{25}{25mV} = -1000$$

- d.) The output resistance for a common-emitter equals  $r_o$ .

$$R_{out} = r_o = \frac{V_A}{I_C} = \frac{25}{100\mu A} = 250k\Omega$$

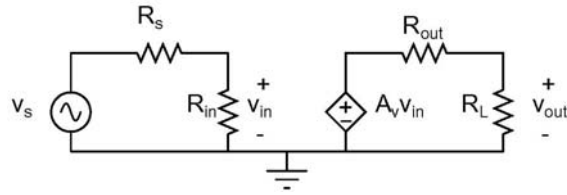- e.) The two-port model is given below. From this model, we can write the overall loaded voltage gain using the voltage-divider rule.



$$\frac{v_{out}}{v_s} = \left( \frac{R_{in}}{R_{in} + R_s} \right) (A_{vo}) \left( \frac{R_L}{R_L + R_{out}} \right)$$

$$\frac{v_{out}}{v_s} = \left( \frac{25\text{k}\Omega}{25\text{k}\Omega + 1\text{k}\Omega} \right) (-1000) \left( \frac{10\text{k}\Omega}{10\text{k}\Omega + 250\text{k}\Omega} \right) = -37$$

- f.) We are given a value of  $\lambda$  at a length of 1.5 $\mu\text{m}$ . Using a length of 1.5 $\mu\text{m}$ , we find that the output resistance is 100k $\Omega$ . We need an output resistance of 250k $\Omega$ , or 2.5 times what is provided by a length of 1.5 $\mu\text{m}$ . Since  $\lambda$  is inversely proportional to length, increasing the length by a factor of 2.5 will result in the necessary output resistance. We need  $L=3.75\mu\text{m}$ .

$$R_{out} = r_o = \frac{1}{\lambda I_D} = 100\text{k}\Omega @ L = 1.5\mu\text{m}$$

- g.) We want to choose  $W$  such that the two amplifiers have the same loaded voltage gain. Since they have equal output resistances and load resistances, the voltage dividers created by  $R_L$  and  $R_{out}$  are equal for both amplifiers. Since the NMOS has infinite input resistance, the voltage divider consisting of  $R_s$  and  $R_{in}$  equals 1 for the NMOS, versus 25/26 for the NPN. We can solve for the necessary  $g_m$  and then the necessary  $W$ .

$$A_v = \frac{25}{26} \cdot 1000 = 961.5 = g_m R_{out} = g_m \cdot 250\text{k}\Omega$$

$$g_m = 0.003846 = \sqrt{2 \cdot \frac{W}{3.75\mu\text{m}} \cdot \frac{50\mu\text{A}}{\text{V}^2} \cdot 100\mu\text{A}}$$

$$W = 5547\mu\text{m}$$

- h.) We want to again bias the amplifier such that all of the  $I_{SUP}$  is sunk by the NMOS. This means that  $I_D = I_{SUP}$ . Since there is infinite input resistance for an NMOS, there is no drop across  $R_s$ .

$$100\mu\text{A} = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2$$

$$V_{GS} = V_T + 0.052\text{V} = 1.052\text{V}$$

$$V_{BIAS} = -2.5\text{V} + V_{GS} = -1.448\text{V}$$

**Problem 2:**

- a.) Here, we find the input resistance, current gain, and output resistance of the common-base amplifier. From the two-port model, we can write the overall current gain  $i_{out}/i_s$ .

$$R_{in} = \frac{1}{g_m} = 125\Omega$$

$$A_i = \frac{\beta}{\beta + 1} = 0.99$$

$$R_{out} = r_o (1 + g_m (r_\pi \parallel R_S)) = 125\Omega (1 + 0.008S (12.5k\Omega \parallel 5k\Omega))$$

$$R_{out} = 3.7M\Omega$$

$$\frac{i_{out}}{i_s} = \left( \frac{R_S}{R_S + R_{in}} \right) (A_i) \left( \frac{R_{out}}{R_L + R_{out}} \right) = 0.975 \cdot 0.99 \cdot 0.987 = 0.953$$

- b.) Here, we find the output resistance and transconductance of the common-emitter amplifier with emitter degeneration. The emitter degeneration resistor is  $R_S$ , since the other current sources are ideal. Since there is no source resistance associated with the voltage source  $v_b$ , the entire voltage  $v_b$  is dropped across  $R_{in}$ .

$$R_{out} = r_o (1 + g_m R_S) = 125k\Omega (1 + 0.008S \cdot 5k\Omega) = 5.125M\Omega$$

$$G_M = \frac{g_m}{1 + g_m R_E} = \frac{0.008S}{1 + 0.008S \cdot 5k\Omega} = 195\mu S$$

$$\frac{i_{out}}{v_b} = -(G_M) \left( \frac{R_{out}}{R_{out} + R_L} \right) = 193\mu S$$

- c.) Here, we rewrite the answers to parts a and b, and divide to find the ratio.

$$i_{out1} = 0.953i_s$$

$$i_{out2} = 0.000193S \cdot v_b$$

$$\frac{i_{out1}}{i_{out2}} = 4938\Omega \cdot \frac{i_s}{v_b}$$

- d.) Increasing  $R_S$  will increase the amount of emitter degeneration. This will decrease the transconductance of the common-emitter amplifier with emitter degeneration, decreasing  $i_{out2}$  and increasing the ratio of part c.

Changing  $R_L$  will have a negligible impact on the ratio in part c, since it only appears in the current-dividers. Since the output resistance of the common base and common emitter amplifiers is very large, the impact of  $R_L$  is insignificant on this ratio.

Finally, increasing  $I_{SUP}$  will increase ratio in part c. Increasing  $I_{SUP}$  has a negligible impact on  $G_M$  of the common-emitter, due to the emitter degeneration. Increasing  $I_{SUP}$  decreases  $R_{in}$  of the common-base, improving the input current-divider, and increasing the ratio in part c.

### Problem 3:

- a.) Due to the backgate effect, we need to find the new  $V_{Tn}$ . After doing this, we can solve for the necessary  $V_{GS}$  such that  $I_D = I_{SUP}$ . Since the source will be at 0V,  $V_{BIAS}$  will equal  $V_{GS}$ .

$$V_{Tn} = V_{Ton} + \gamma_n \left( \sqrt{-V_{BS} - 2\Phi_p} - \sqrt{-2\Phi_p} \right)$$

$$V_{Tn} = 0.7V + 0.5 \left( \sqrt{2.5 + 0.8} - \sqrt{0.8} \right) = 1.16V$$

$$200\mu A = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2$$

$$V_{BIAS} = V_{GS} = V_T + 0.4V = 1.56V$$

- b.) The minimum  $V_{OUT}$  is determined by the voltage requirement across the current source. Since the current source needs 0.5V across it,  $V_{OUT, min} = -2.0V$ . The maximum  $V_{OUT}$  is one  $V_{DS, sat}$  from the positive rail. However, the value of  $V_{DS, sat}$  depends on the maximum  $V_{OUT}$ , since at this point, the drain current is not necessarily equal to  $I_{SUP}$ .

$$I_D = I_{SUP} + I_{OUT} = I_{SUP} + \frac{V_{OUT}}{R_L}$$

$$V_{DS, sat} = V_{GS} - V_{Tn} = \sqrt{\frac{I_D}{\frac{W}{2L} \mu_n C_{ox}}} = \sqrt{\frac{I_{SUP} + \frac{V_{OUT}}{R_L}}{\frac{W}{2L} \mu_n C_{ox}}}$$

$$V_{OUT} = V_{DD} - V_{DS, sat} = V_{DD} - \sqrt{\frac{I_{SUP} + \frac{V_{OUT}}{R_L}}{\frac{W}{2L} \mu_n C_{ox}}}$$

$$V_{OUT} = 2.08V$$

- c.) The overall voltage gain can be found by inspecting  $R_{in}$ ,  $A_{vo}$ , and  $R_{out}$ . Due to the backgate effect, the backgate transconductance  $g_{mb}$  must also be calculated.

$$R_{in} = \infty$$

$$A_{vo} = \frac{g_m}{g_m + g_{mb}}$$

$$g_{mb} = g_m \left( \frac{\gamma_n}{2\sqrt{-2\Phi_p - V_{BS}}} \right) = g_m \left( \frac{0.5}{2\sqrt{2.5 + 0.8}} \right) = g_m (0.138)$$

$$A_{vo} = \frac{1}{1 + 0.138} = 0.879$$

$$R_{out} = \frac{1}{g_m + g_{mb}} = \frac{1}{g_m (1.138)}$$

$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D} = 0.001$$

$$R_{out} = 879 \Omega$$

$$\frac{v_{out}}{v_s} = (A_{vo}) \left( \frac{R_L}{R_L + R_{out}} \right) = 0.879 \cdot \left( \frac{100k\Omega}{100k\Omega + 879\Omega} \right) = 0.871$$

- d.) Repeating parts a-c, we first solve for the necessary bias voltage. With no backgate effect, the threshold voltage is lower.

$$V_{Tn} = V_{Ton} = 0.7V$$

$$200\mu A = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2$$

$$V_{BIAS} = V_{GS} = V_T + 0.4V = 1.1V$$

Next we check the minimum and maximum  $V_{OUT}$ . The minimum  $V_{OUT}$  remains unchanged, and is still determined by the voltage requirement of the current source. The maximum  $V_{OUT}$  also remains unchanged, since the equation that needed to be solved for  $V_{OUT}$  is independent of  $V_{Tn}$ . Finally, we solve for the the gain, with the backgate transconductance generator turned off. Note that the gain is much higher when there is no backgate effect.

$$R_{in} = \infty$$

$$A_{vo} = 1$$

$$R_{out} = \frac{1}{g_m} = 1k\Omega$$

$$\frac{v_{out}}{v_s} = (A_{vo}) \left( \frac{R_L}{R_L + R_{out}} \right) = 1 \cdot \left( \frac{100k\Omega}{100k\Omega + 1k\Omega} \right) = 0.99$$