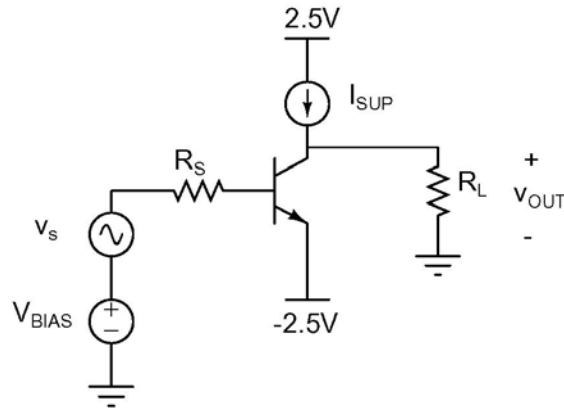


Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.012 Microelectronic Devices and Circuits
Spring 2007

Homework #8 – Due May 11, 2007


Problem 1:



Device Parameters	
$I_{SUP}=100\mu A$	$I_S=10^{-15} A$
$R_S=5k\Omega$	$\beta_F=\beta_o=100$
$R_L=10k\Omega$	$V_A=100V$
$r_{oc}=\infty$	$f_T=1GHz @ I_C=100\mu A$
	$C_\mu=0.1pF$

- a.) Calculate V_{BIAS} such that $V_{OUT}=0V$.
- b.) Calculate the low frequency loaded voltage gain v_{out}/v_s .
- c.) Calculate C_π from the device data.
- d.) Use the Miller approximation to calculate ω_{3db} .
- e.) Use the open-circuit time constant method to calculate ω_{3db} .

Problem 2:

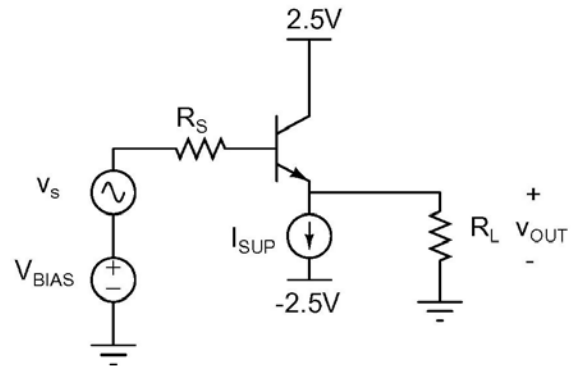


Device Parameters	
$R_L=25k\Omega$	$C_{je0}=100fF$
$R_S=5k\Omega$	$\tau_F=100ps$
$I_S=10^{-15}A$	$C_{\mu0}=200fF$
$\beta_F=\beta_o=100$	$r_{oc}=\infty$
$V_A=100V$	$\Phi_{Bc}=0.75V$

In the previous problem, the high source resistance lowered ω_{3db} . One method of improving the frequency response is to precede the common emitter stage with an emitter-follower stage.

- Find I_{SUP} for the emitter follower such that its R_{out} equals 100Ω .
- Calculate V_{BIAS} such that $V_{OUT}=0V$.
- Calculate C_{π} and C_{μ} from the device data for the emitter-follower.
- Use the open-circuit time constant method to calculate ω_{3db} for the emitter-follower.

Problem 3:

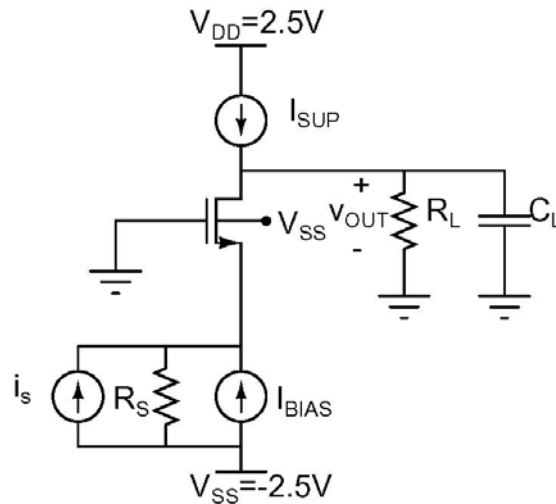

Device Parameters	
$R_S=100\text{k}\Omega$	$\mu_n C_{ox}=50\text{uA/V}^2$
$R_L=1\text{k}\Omega$	$C_{ox}=2.3\text{fF/um}^2$
$r_{oc}=\infty$	$C_{Jn}=0.1\text{fF/um}^2$
$V_{Tn}=1\text{V}$	$C_{JSWn}=0.5\text{fF/um}$
$\lambda_n=0.05\text{V}^{-1}$	$L_{diffn}=6\text{um}$
$C_L=0.5\text{pF}$	$C_{ov}=0.5\text{fF/um}$

The frequency response of the NMOS common-gate amplifier depends on g_m , C_{gs} , C_{gd} , and C_L . One method of increasing g_m is to increase the bias current. Another method of increasing g_m is to increase the W of the device. However, as the width of the device is increased, the parasitic capacitances also increase. For this problem, include C_{db} , but neglect the backgate effect. Assume that the amplifier is biased such that $V_{OUT}=0\text{V}$.

- Use the open-circuit time constant method to derive an expression for ω_{3db} for the common-gate amplifier including C_L .
- Use Matlab or Excel to plot ω_{3db} vs. I_{SUP} for $50\text{uA} < I_{SUP} < 500\text{uA}$. Use $W/L=50\text{um}/2\text{um}$.
- What is the effect of increasing I_{SUP} (for a constant W) on the frequency response of this amplifier? What are some potential drawbacks of this approach?