

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.012 Microelectronic Devices and Circuits  
Spring 2007

Homework #8 – Due May 11, 2007

**Problem 1:**

- a.) To obtain  $V_{OUT}=0V$ , we need  $I_{OUT}=0A$ , so  $I_C$  must equal  $I_{SUP}$ . Using this information, we can calculate  $V_{BE}$  as well as the voltage drop across  $R_S$ . Adding these drops to the negative voltage supply yields the necessary  $V_{BIAS}$ .

$$V_{BE} = V_{th} \ln\left(\frac{I_C}{I_S}\right) = 0.025 \cdot \ln\left(\frac{100\mu A}{1fA}\right) = 633mV$$

$$I_B R_S = 1\mu A \cdot 5k\Omega = 5mV$$

$$V_{BIAS} = -2.5 + I_B R_S + V_{BE} = -1.862V$$

- b.) The input resistance, unloaded voltage gain, and output resistance are given below.

$$R_{in} = r_{\pi} = 25k\Omega$$

$$A_{vo} = \frac{-V_A}{V_{th}} = -4000$$

$$R_{out} = \frac{V_A}{I_C} = 1M\Omega$$

$$A_v = \left(\frac{R_{in}}{R_{in} + R_S}\right) A_{vo} \left(\frac{R_L}{R_L + R_{out}}\right) = -33$$

- c.) Using the given  $f_T$ ,  $I_{SUP}$  and  $C_{\mu}$ , we can solve for  $C_{\pi}$ .

$$\omega_T = 2\pi f_T = \frac{g_m}{C_{\pi} + C_{\mu}}$$

$$6.28e9 \text{ rad/s} = \frac{0.004S}{C_{\pi} + 100fF}$$

$$C_{\pi} = 536fF$$

d.) In the Miller approximation,  $C_\mu$  is Miller-multiplied, to form a large equivalent capacitance. The resulting  $\omega_{3db}$  is given below.

$$\omega_{3db} = \frac{1}{R'_in} \left[ \frac{1}{C_\pi + (1 + g_m R'_{out}) C_\mu} \right]$$

$$R'_{out} = r_o \parallel R_L = 9.9\text{k}\Omega$$

$$R'_in = R_s \parallel r_\pi = 4.2\text{k}\Omega$$

$$\omega_{3db} = 5.22\text{e}7 \text{ rad/s}$$

e.) There are two open circuit time constants due to the two parasitic capacitances. The inverse of the time-constant sum yields the 3db bandwidth.

$$\omega_{3db} = \frac{1}{\tau_\pi + \tau_\mu}$$

$$\tau_\pi = R'_in C_\pi = 2.2\text{ns}$$

$$\tau_\mu = (R'_{out} + R'_in (1 + g_m R'_{out})) C_\mu = 17.9\text{ns}$$

$$\omega_{3db} = 4.96\text{e}7 \text{ rad/s}$$

**Problem 2:**

- a.) Given a source resistance and  $\beta$ , we can solve for the necessary  $I_C$  such that the total output resistance is 100 ohms.

$$R_{out} = \frac{1}{g_m} + \frac{R_s}{\beta} = 100\Omega$$

$$\frac{1}{g_m} = 50\Omega$$

$$I_C = 500\mu\text{A}$$

- b.) The necessary bias voltage equals  $V_{BE}$  plus any drop across the source resistance.

$$V_{BIAS} = I_B R_s + V_{th} \ln\left(\frac{I_C}{I_S}\right) = 25\text{mV} + 673\text{mV} = 698\text{mV}$$

- c.)  $C_\pi$  and  $C_\mu$  can be found from device parameters.

$$C_\pi = g_m \tau_f + \sqrt{2} C_{je0} = 2.14\text{pF}$$

$$C_\mu = \frac{C_{\mu0}}{\sqrt{1 + \frac{V_{CB}}{\Phi_{Bc}}}} = \frac{200\text{fF}}{\sqrt{1 + \frac{2.5 - 0.698}{0.75}}} = 108\text{fF}$$

- d.) We use the Miller approximation and open-circuit time constants to find the 3db bandwidth of the common-collector.

$$C_T = C_\pi \left( \frac{1/g_m}{1/g_m + R_L} \right) + C_\mu = 112\text{fF}$$


$$R_T = R_s \parallel R_{in} = 5\text{k}\Omega \parallel (r_\pi + (\beta + 1)R_L) = 5\text{k}\Omega$$

$$\tau = R_T C_T = 0.56\text{ns}$$

$$\omega_{3\text{db}} = \frac{1}{\tau} = 1.8\text{e}9 \text{ rad/s}$$

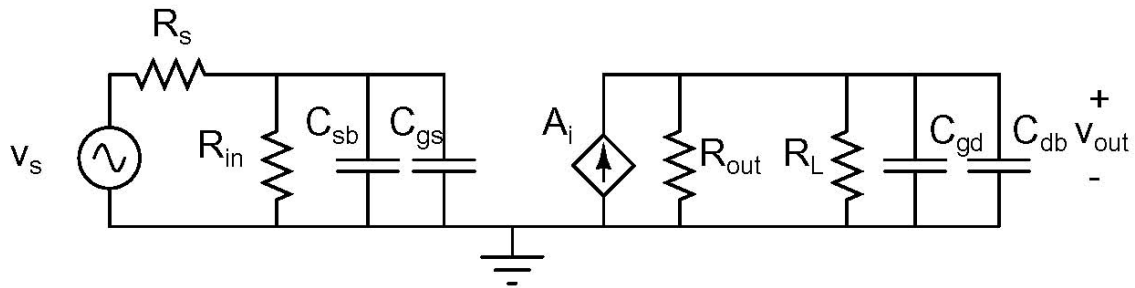**Problem 3:**

- a.) Since the bulk is tied to a DC potential,  $C_{db}$  appears between the drain and AC ground. The relevant two-port model is given below. Students did not need to consider  $C_{sb}$ , although its position is shown in the two-port model. The rest of the problem ignores  $C_{sb}$ . In addition, we use the zero-bias value of  $C_{db}$  which gives a conservative estimate of the 3db bandwidth.



$$R'_{in} = R_s \parallel \frac{1}{g_m}$$

$$R'_{out} = R_L \parallel r_o (1 + g_m R_s)$$


$$\omega_{3db} = \frac{1}{C_{gs} R'_{in} + (C_{gd} + C_{db}) R'_{out}}$$

- b.) The relevant formulas for the parasitic capacitances are given below. As mentioned above, we ignored  $C_{sb}$ , and used the zero-bias value for  $C_{db}$ .

$$C_{gs} = \frac{2}{3} W L C_{ox} + W C_{ov} = 178 \text{fF}$$

$$C_{gd} = W C_{ov} = 25 \text{fF}$$
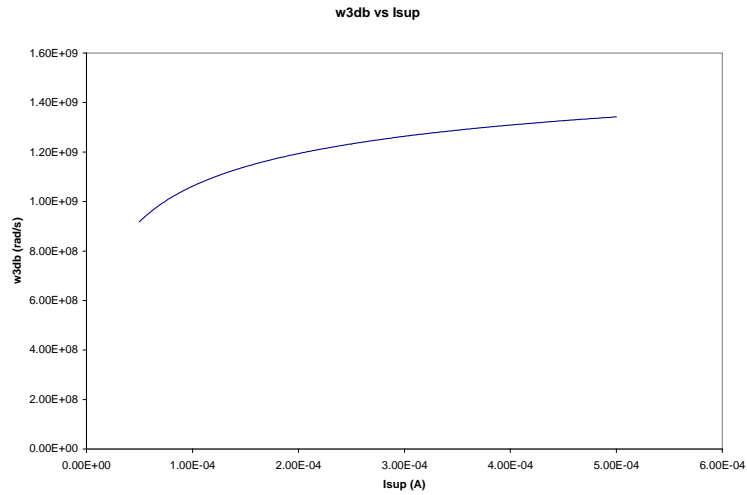
$$C_{db} = C_j W L_{diff} + C_{jsw} (W + 2L_{diff}) = 61 \text{fF}$$



- c.) Increasing  $I_{SUP}$  improves the frequency response of the amplifier by minimizing the time constant due to  $C_{gs}$ . However, as  $I_{SUP}$  increases, the dominant time constant becomes the one due to  $C_{gd}$  and  $C_{db}$ . Since the equivalent resistance associated with these capacitors is  $R_L$  due to the high output resistance of the common-gate stage, increasing  $I_{SUP}$  does not modify these time constants. Increasing  $I_{SUP}$  has the drawback of increased power dissipation with diminishing returns.