


L10: Analog Building Blocks

(OpAmps, A/D, D/A)



Acknowledgement: Dave Wentzloff



DC Model

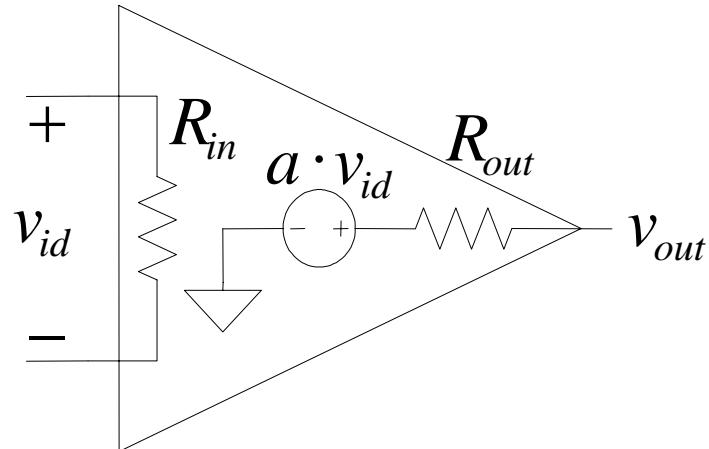


- Typically very high input resistance $\sim 300\text{K}\Omega$
- High DC gain ($\sim 10^5$)
- Output resistance $\sim 75\Omega$

$$V_{out} = a(f) \cdot V_{in}$$



LM741 Pinout

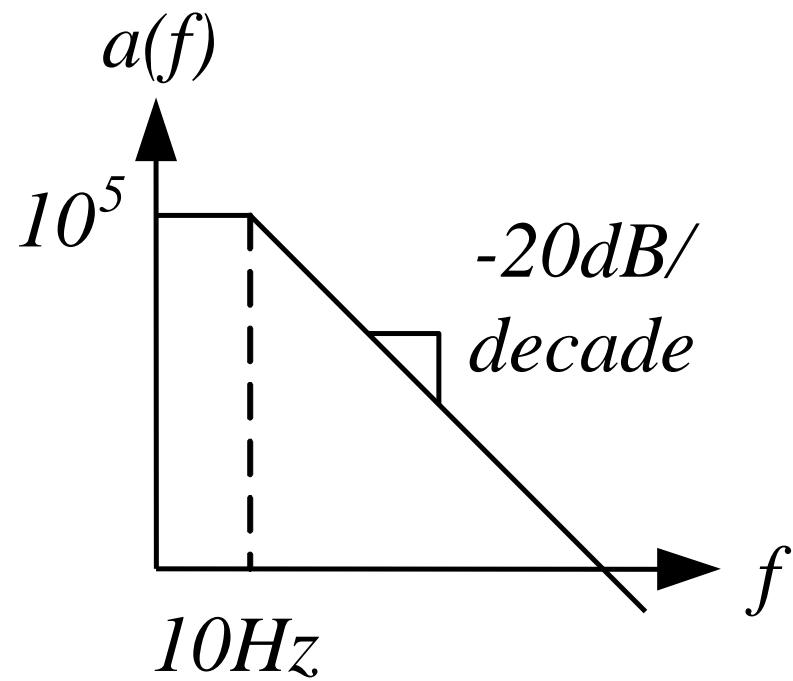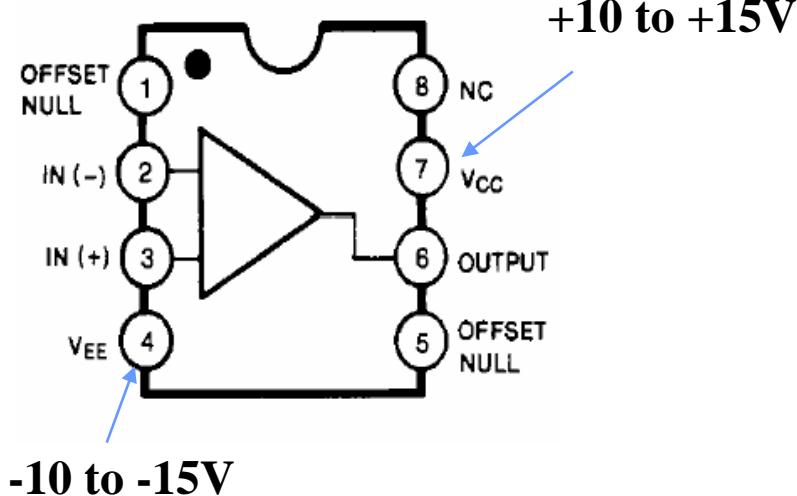

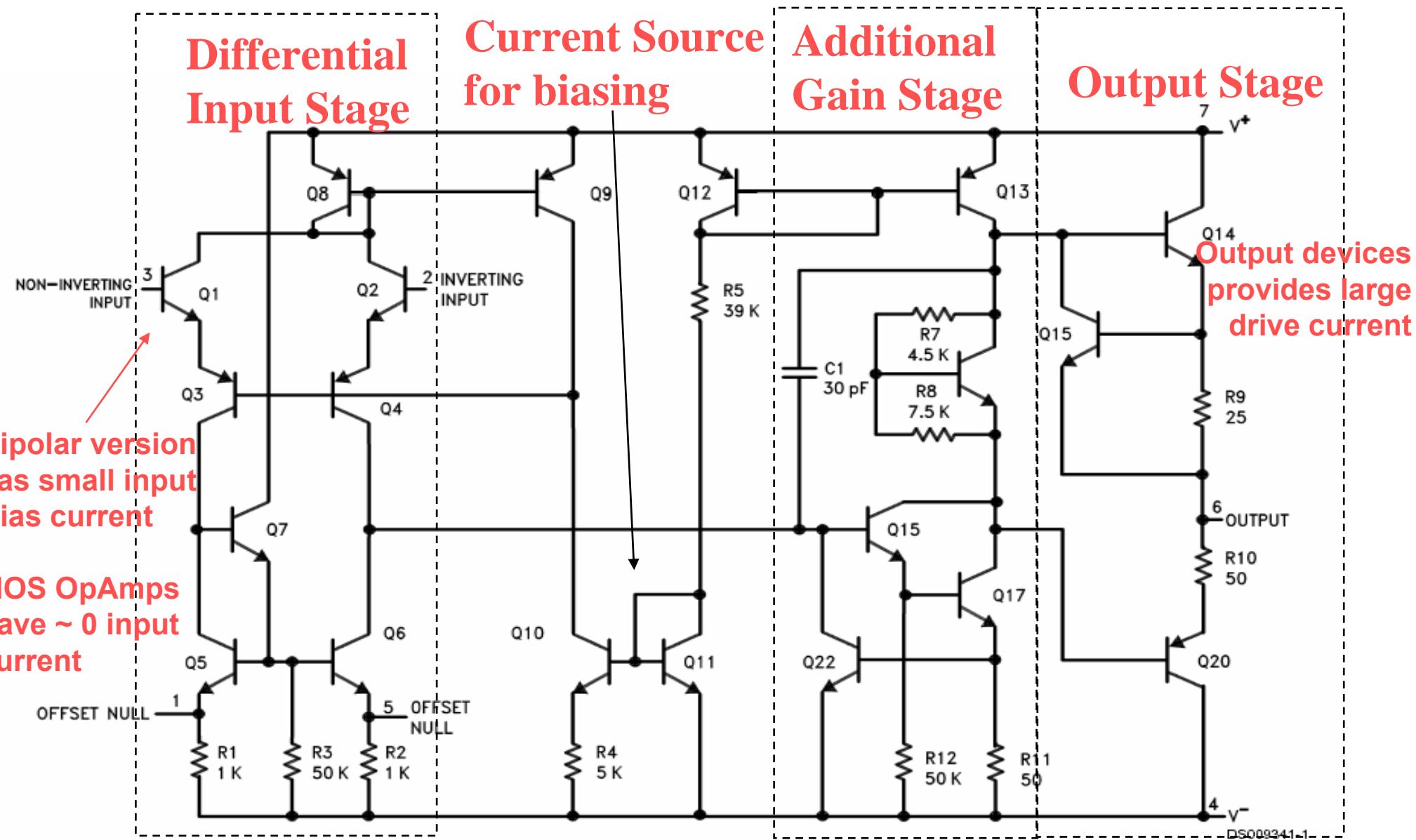


**Gain is Sensitive to Operating Condition
(e.g., Device, Temperature, Power supply voltage, etc.)**

Simple Model for an OpAmp

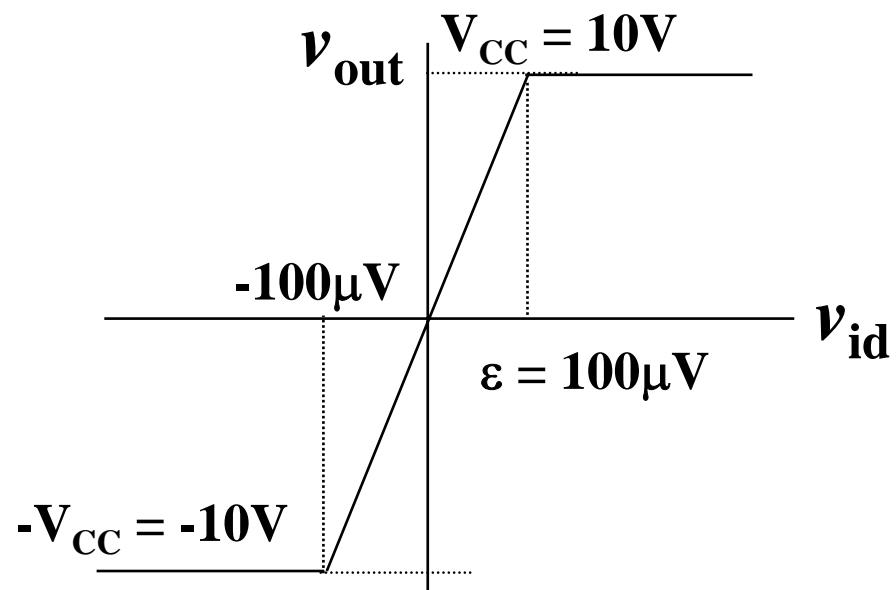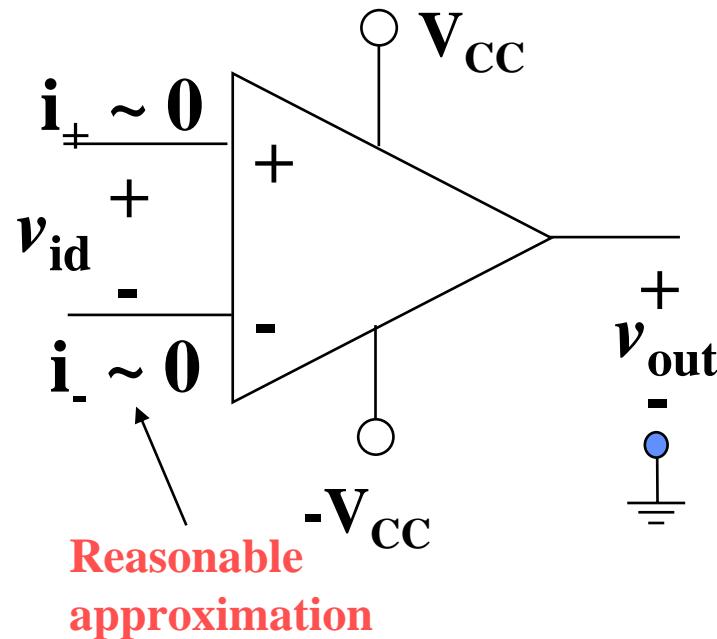


Linear Mode

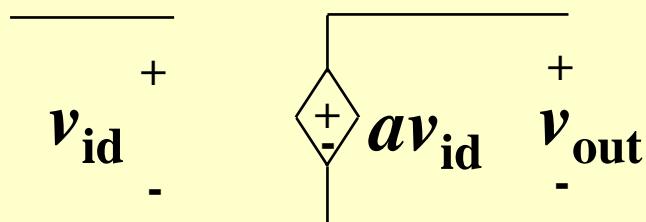


If $-V_{CC} < v_{out} < V_{CC}$

Negative Saturation

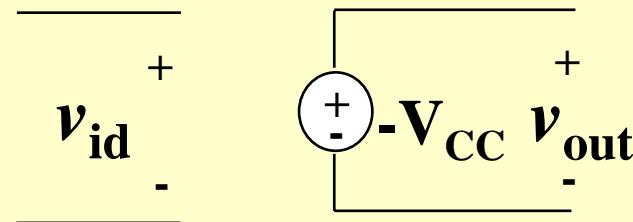


$v_{id} < -\varepsilon$

Positive Saturation

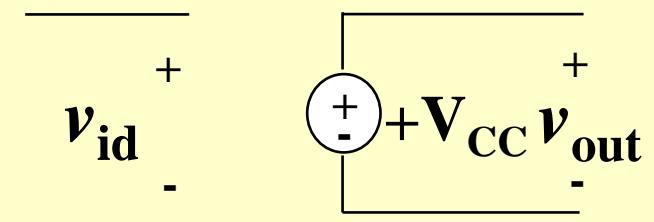

$v_{id} > \varepsilon$

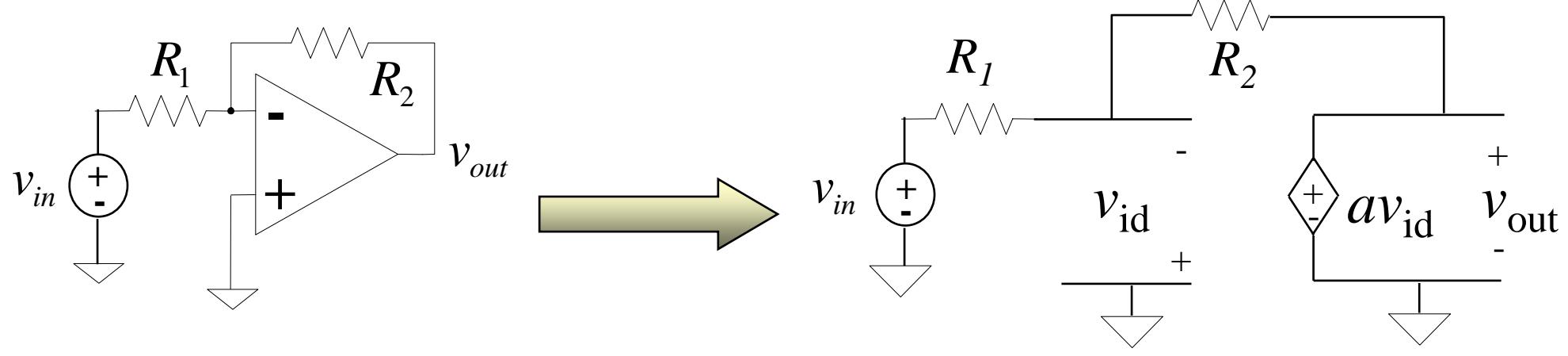Small input range for “Open” loop Configuration



$$\frac{v_{in} + v_{id}}{R_1} + \frac{v_{out} + v_{id}}{R_2} = 0$$


$$v_{id} = \frac{v_{out}}{a}$$

$$\frac{v_{in}}{R_1} = -\frac{v_{out}}{a} \left[\frac{1}{R_1} + \frac{a}{R_2} + \frac{1}{R_2} \right]$$

$$\frac{v_{out}}{v_{in}} = -\frac{R_2 a}{(1+a)R_1 + R_2} \approx -\frac{R_2}{R_1} \quad (\text{if } a \gg 1)$$


- Overall (closed loop) gain does not depend on open loop gain
- Trade gain for robustness
- Easier analysis approach: “virtual short circuit approach”
 - $v_+ = v_- = 0$ if OpAmp is linear

Voltage Follower (buffer)

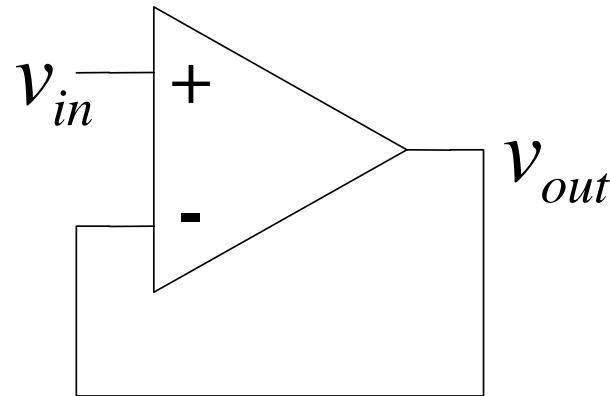


$$v_{out} \approx v_{in}$$

Differential Input

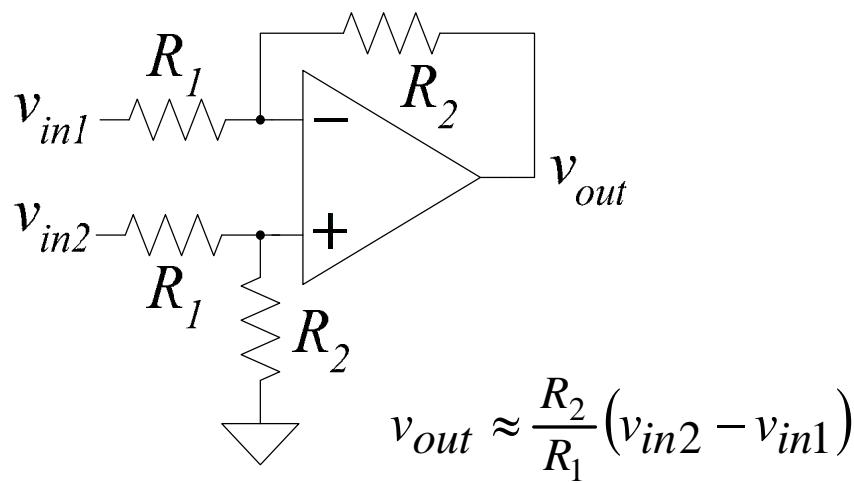


$$v_{out} \approx \frac{R_2}{R_1} (v_{in2} - v_{in1})$$

Non-inverting

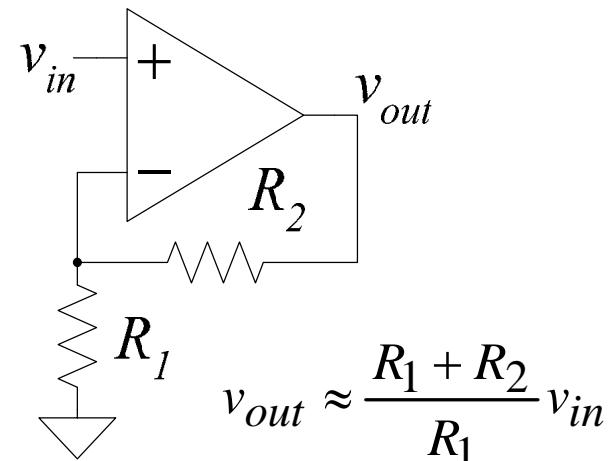

$$v_{out} \approx \frac{R_1 + R_2}{R_1} v_{in}$$

Integrator

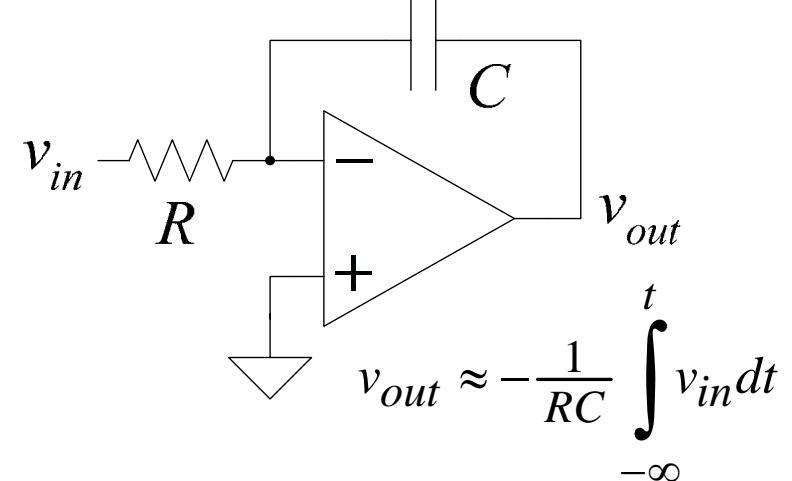

$$v_{out} \approx -\frac{1}{RC} \int_{-\infty}^t v_{in} dt$$


Analog Comparator:

Is $V_+ > V_-$?




The Output is a DIGITAL signal

Analog Comparator: Analog to TTL


LM 311 Needs Pull-Up

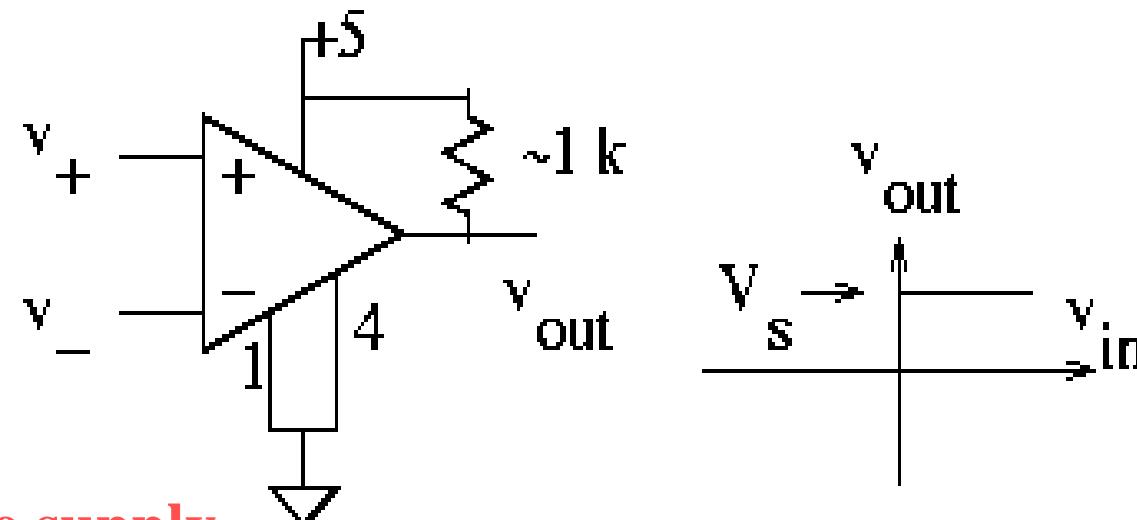

LM311 is a single supply
comparator

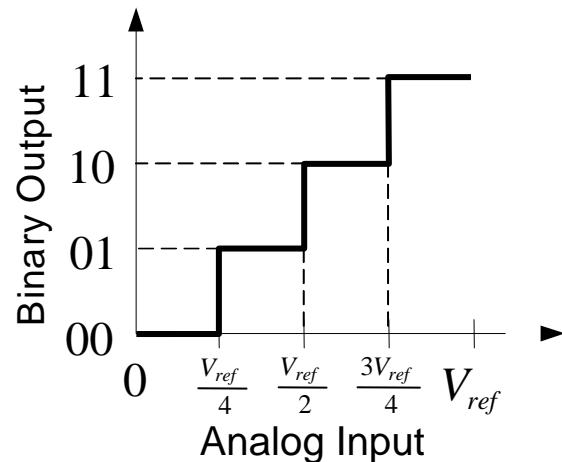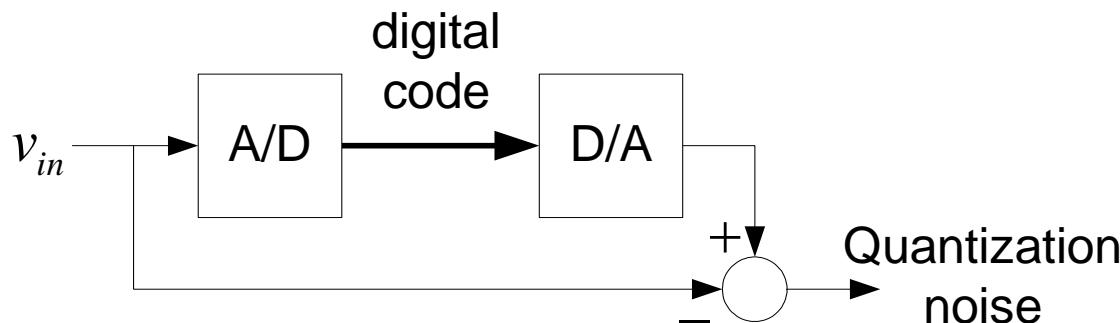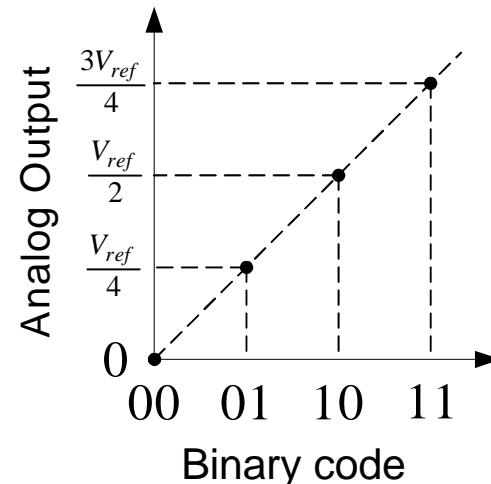
A/D Conversion**D/A Conversion**

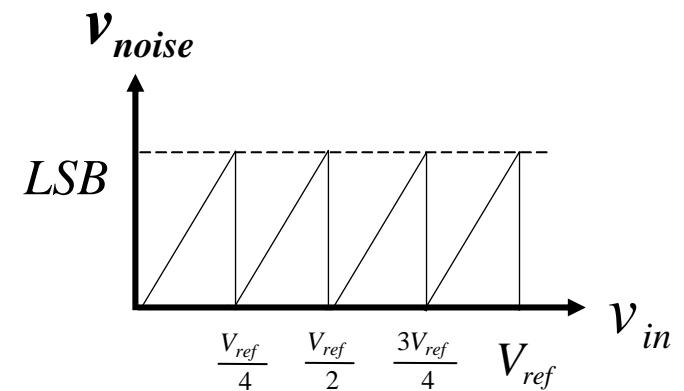- Quantization noise exists even with *ideal A/D and D/A converters*




Non-idealities in Data Conversion

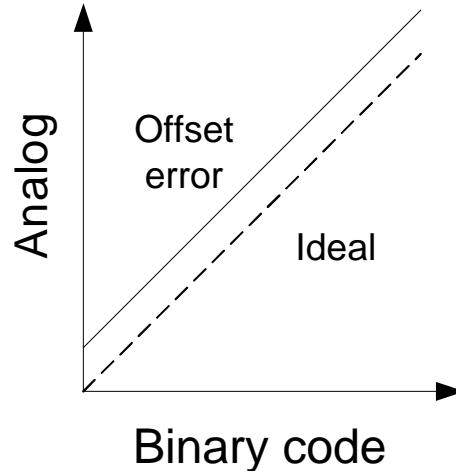
Offset – a constant voltage offset that appears at the output when the digital input is 0



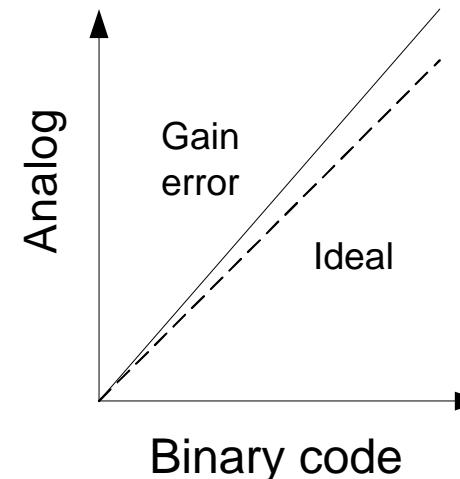
Gain error – deviation of slope from ideal value of 1




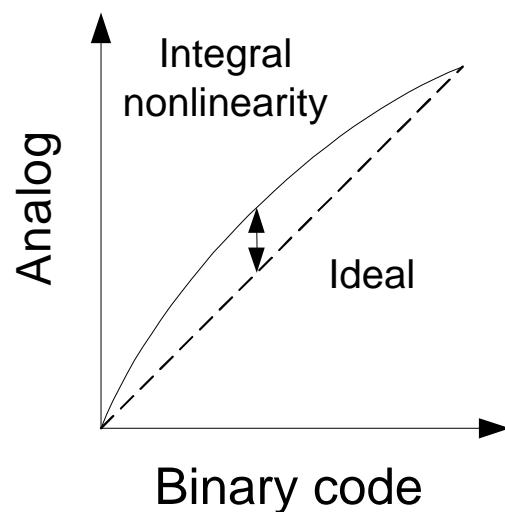Integral Nonlinearity – maximum deviation from the ideal analog output voltage



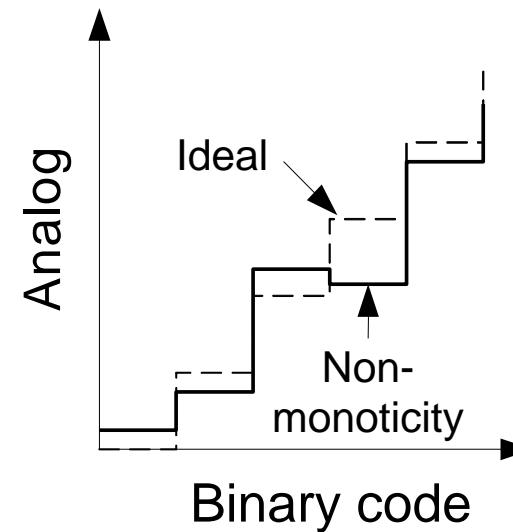
Differential nonlinearity – the largest increment in analog output for a 1-bit change



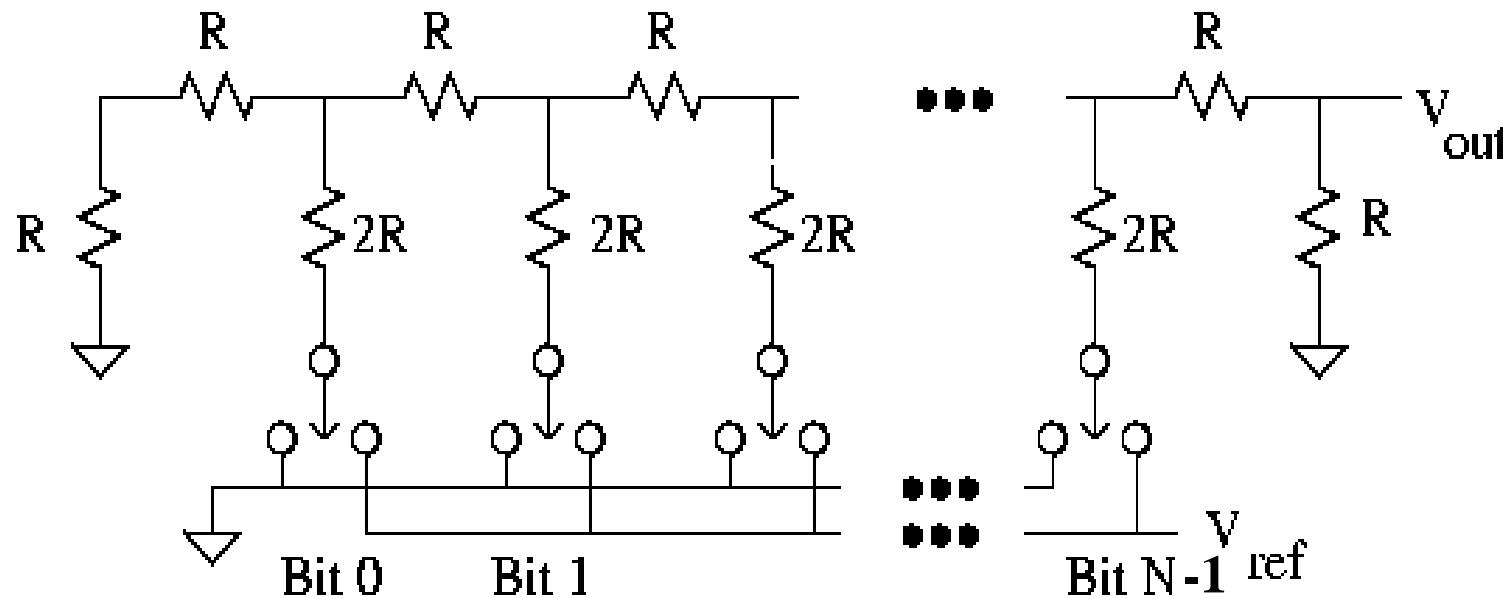

$$V_{\text{out}} = \frac{1}{6} V_{\text{ref}} [B_7 + \frac{1}{2}B_6 + \frac{1}{4}B_5 + \dots + \frac{1}{128}B_0]$$

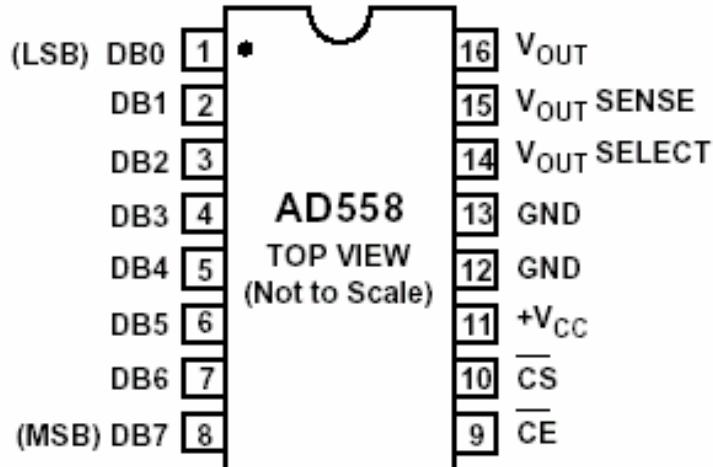- Note that the driving point impedance (resistance) is the same for each cell.
- R-2R Ladder achieves large current division ratios with only two resistor values



Input Logic Coding

Digital Input Code		Output Voltage		
Binary	Hexadecimal	Decimal	2.56 V Range	10.000 V Range
0000 0000	00	0	0	0
0000 0001	01	1	0.010 V	0.039 V
0000 0010	02	2	0.020 V	0.078 V
0000 1111	0F	15	0.150 V	0.586 V
0001 0000	10	16	0.160 V	0.625 V
0111 1111	7F	127	1.270 V	4.961 V
1000 0000	80	128	1.280 V	5.000 V
1100 0000	C0	192	1.920 V	7.500 V
1111 1111	FF	255	2.55 V	9.961 V

- 8-bit DAC
- Single Supply Operation: 5V to 15V
- Integrates required references (bandgap voltage reference)
- Uses a R-2R resistor ladder
- Settling time 1µs
- Programmable output range from 0V to 2.56V or 0V to 10V
- Simple Latch based interface

Chip Architecture and Interface

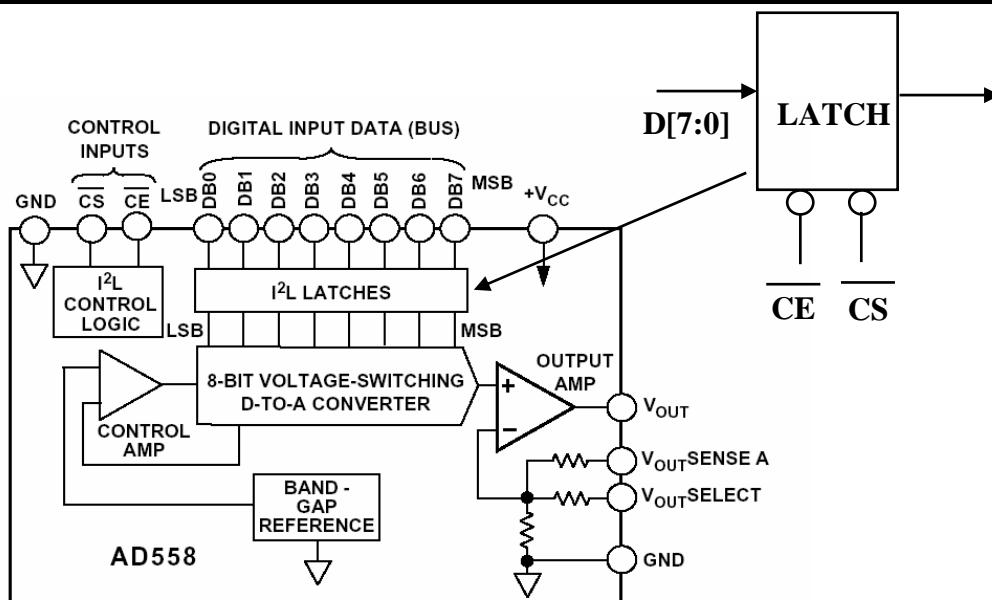



Table I. AD558 Control Logic Truth Table

Input Data	\overline{CE}	\overline{CS}	DAC Data	Latch Condition
0	0	0	0	"Transparent"
1	0	0	1	"Transparent"
0	g	0	0	Latching
1	g	0	1	Latching
0	0	g	0	Latching
1	0	g	1	Latching
X	1	X	Previous Data	Latched
X	X	1	Previous Data	Latched

NOTES

X = Does not matter.

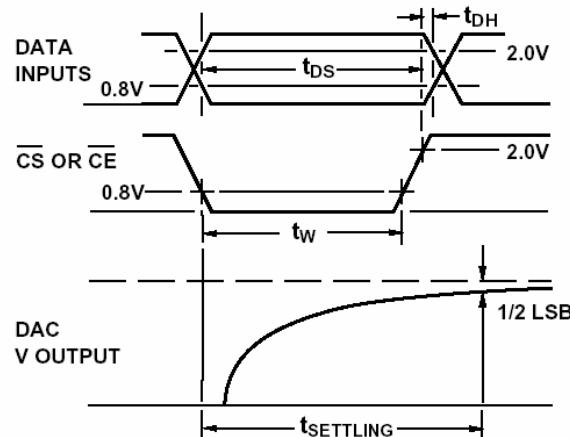g = Logic Threshold at Positive-Going Transition.



t_W = STORAGE PULSE WIDTH = 200ns MIN

t_{DH} = DATA HOLD TIME = 10ns MIN

t_{DS} = DATA SETUP TIME = 200ns MIN

$t_{SETTLING}$ = DAC OUTPUT SETTLING TIME TO $\pm 1/2$ LSB

Outputs are noisy
when input bits settle,
so it is best to have inputs
stable before latching
the input data


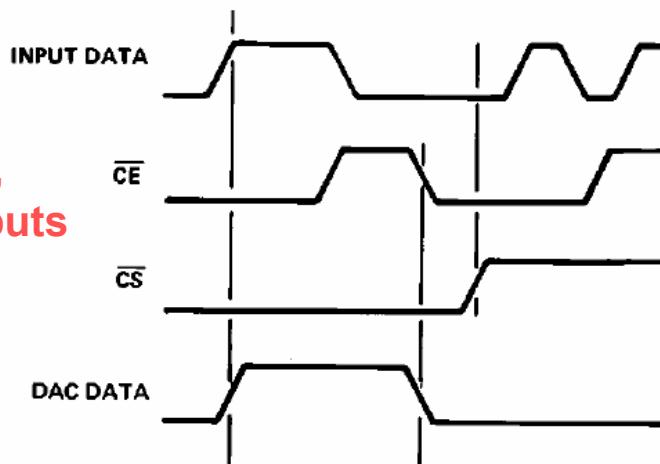


Figure 6. AD558 Control Logic Function

Setting the Voltage Range

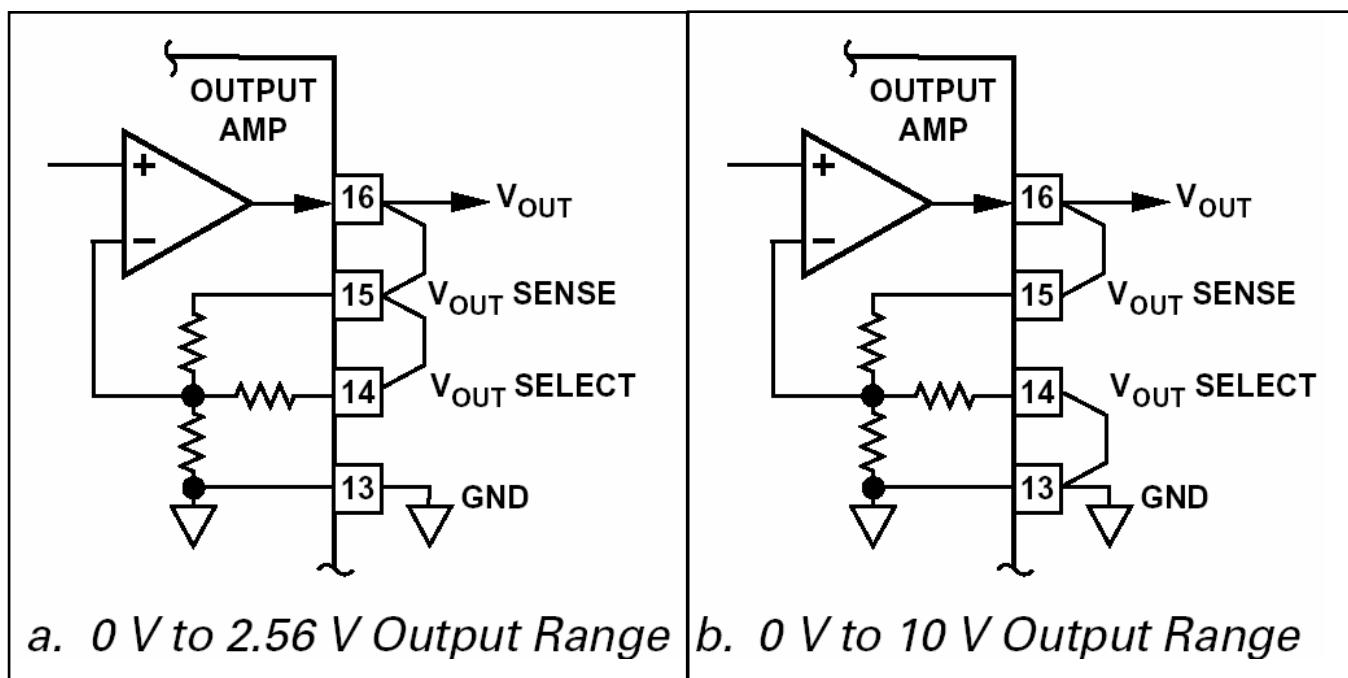


Very similar to a
non-inverting amp

Strap output for
different voltage
ranges


Input Logic Coding

Digital Input Code			Output Voltage	
Binary	Hexadecimal	Decimal	2.56 V Range	10.000 V Range
0000 0000	00	0	0	0
0000 0001	01	1	0.010 V	0.039 V
0000 0010	02	2	0.020 V	0.078 V
0000 1111	0F	15	0.150 V	0.586 V
0001 0000	10	16	0.160 V	0.625 V
0111 1111	7F	127	1.270 V	4.961 V
1000 0000	80	128	1.280 V	5.000 V
1100 0000	C0	192	1.920 V	7.500 V
1111 1111	FF	255	2.55 V	9.961 V

Convert data to
Offset binary

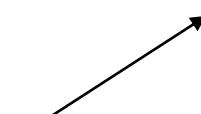


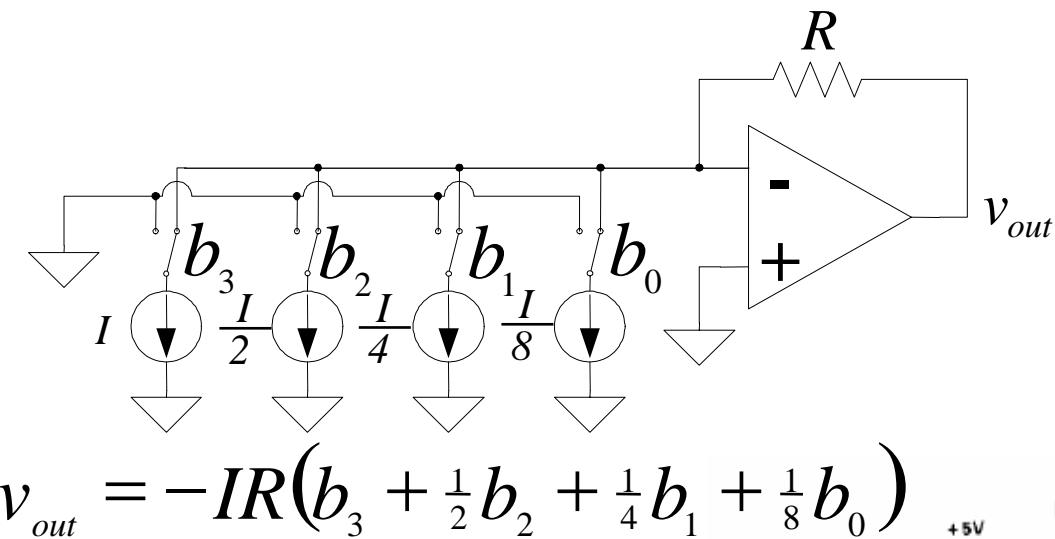MIT Another Approach: Binary-Weighted DAC MIT




- Switch binary-weighted currents
- MSB to LSB current ratio is 2^N

AD9768

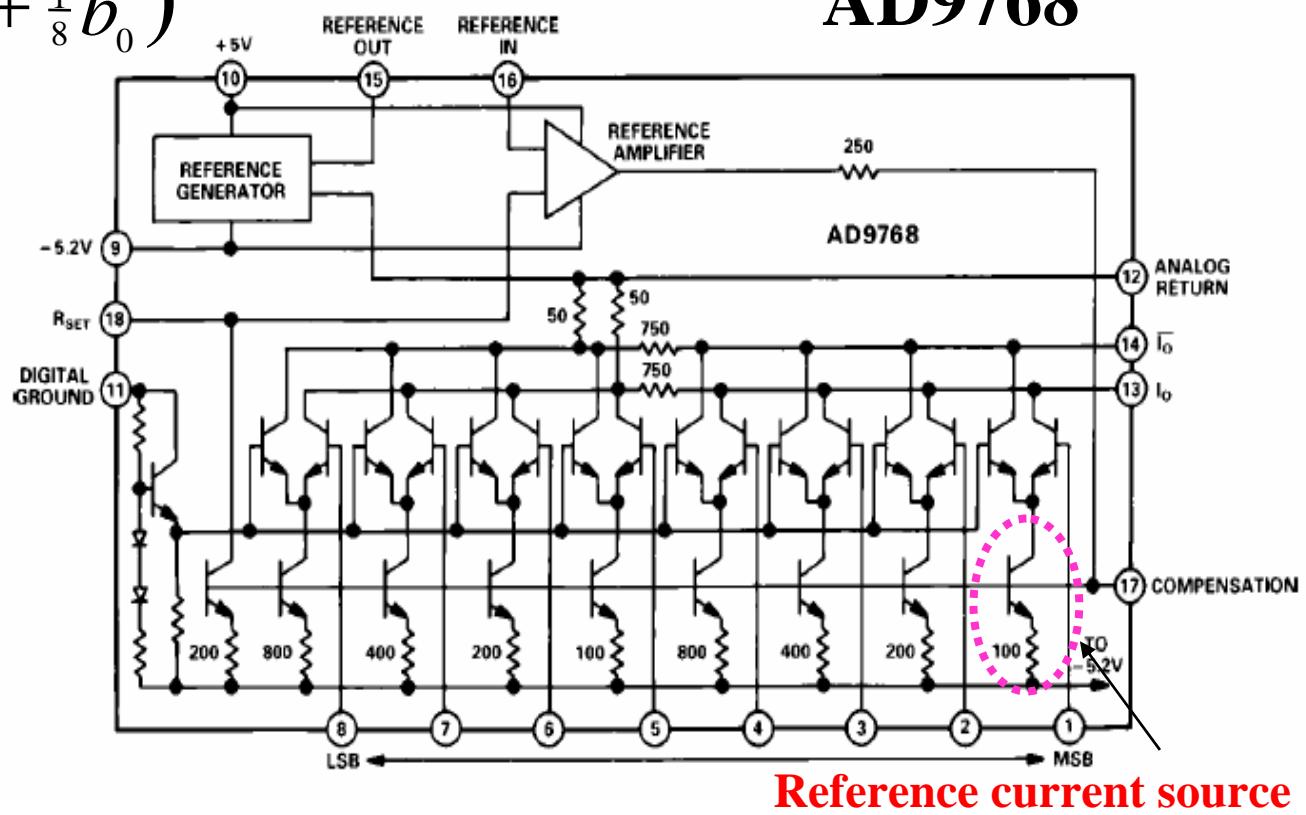


Reference current source


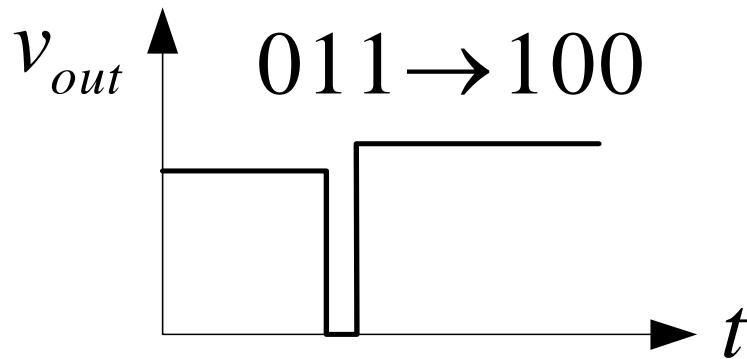
- Glitching is caused when switching times in a D/A are not synchronized
- Example: Output changes from 011 to 100 – MSB switch is delayed
- Filtering reduces glitch but increases the D/A settling time
- One solution is a thermometer code D/A – requires $2^N - 1$ switches but no ratioed currents




Binary	Thermometer
0 0	0 0 0
0 1	0 0 1
1 0	0 1 1
1 1	1 1 1

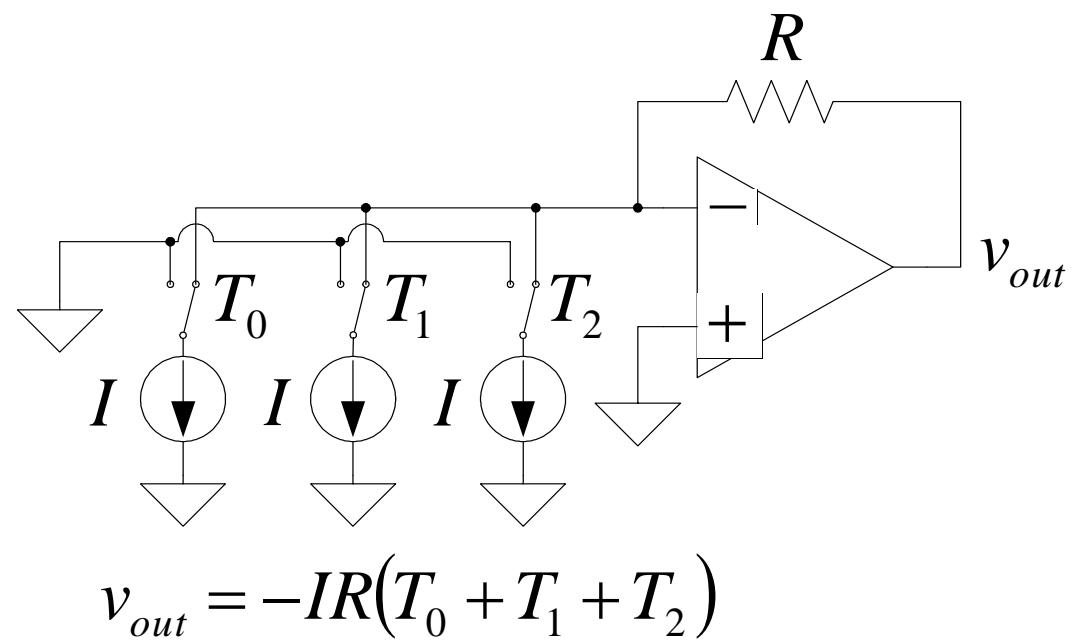

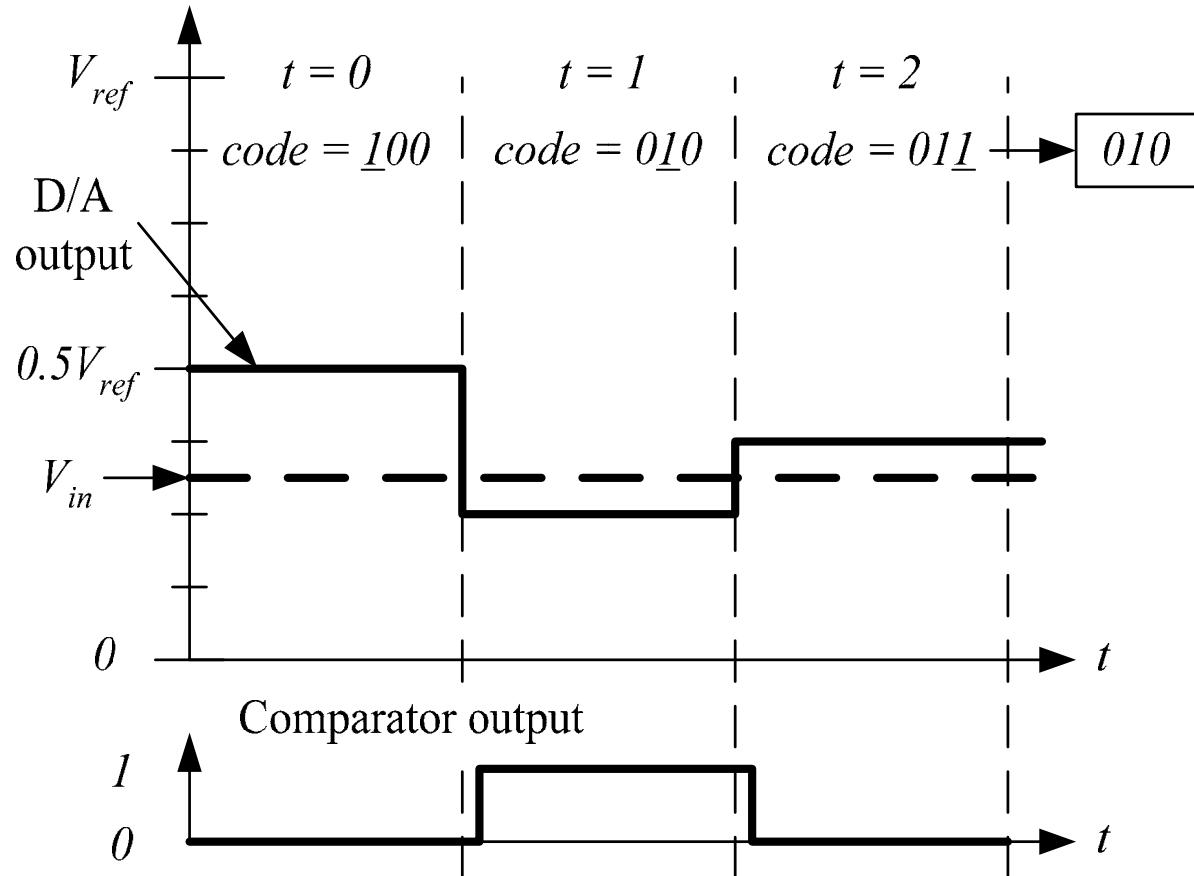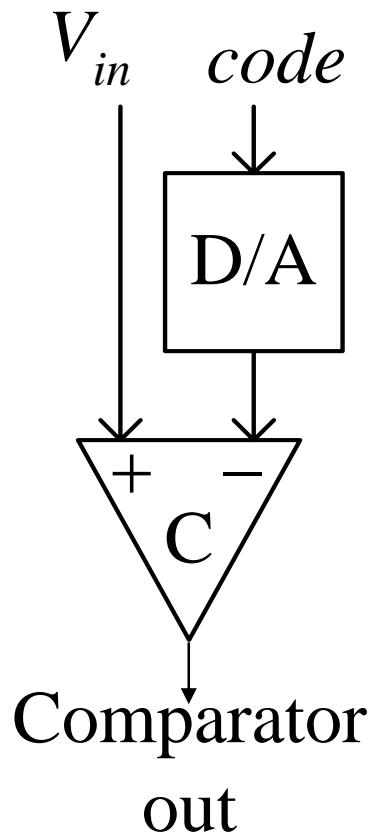- D/A converters are typically compact and easier to design. Why not A/D convert using a D/A converter and a comparator?
- D to A generates analog voltage which is compared to the input voltage
- If D to A voltage > input voltage then set that bit; otherwise, reset that bit
- This type of A to D takes a fixed amount of time proportional to the bit length




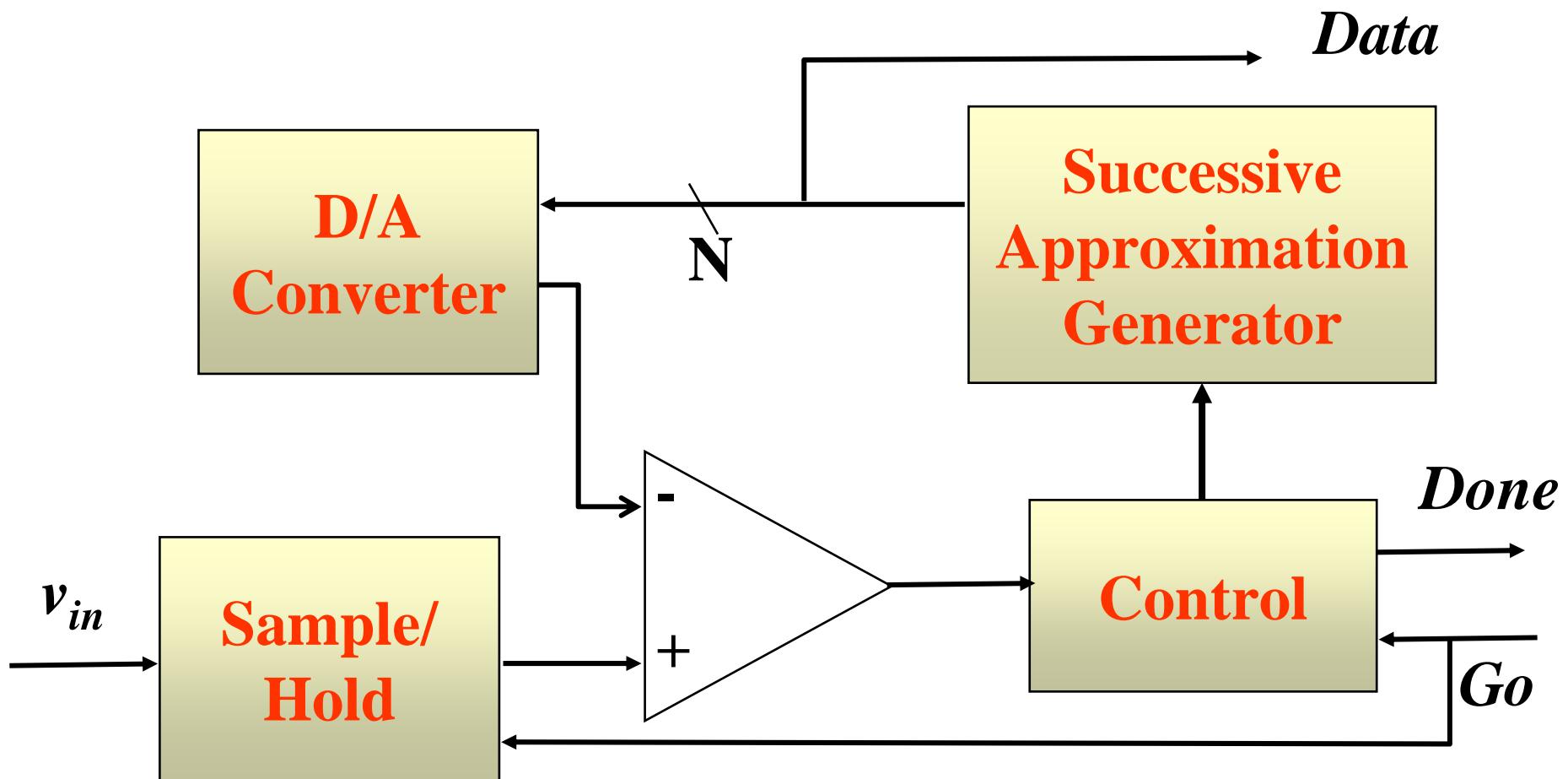Example: 3-bit A/D conversion, $2 \text{ LSB} < V_{in} < 3 \text{ LSB}$




- Serial conversion takes a time equal to $N(t_{D/A} + t_{comp})$

Successive-Approximation A/D (AD670)

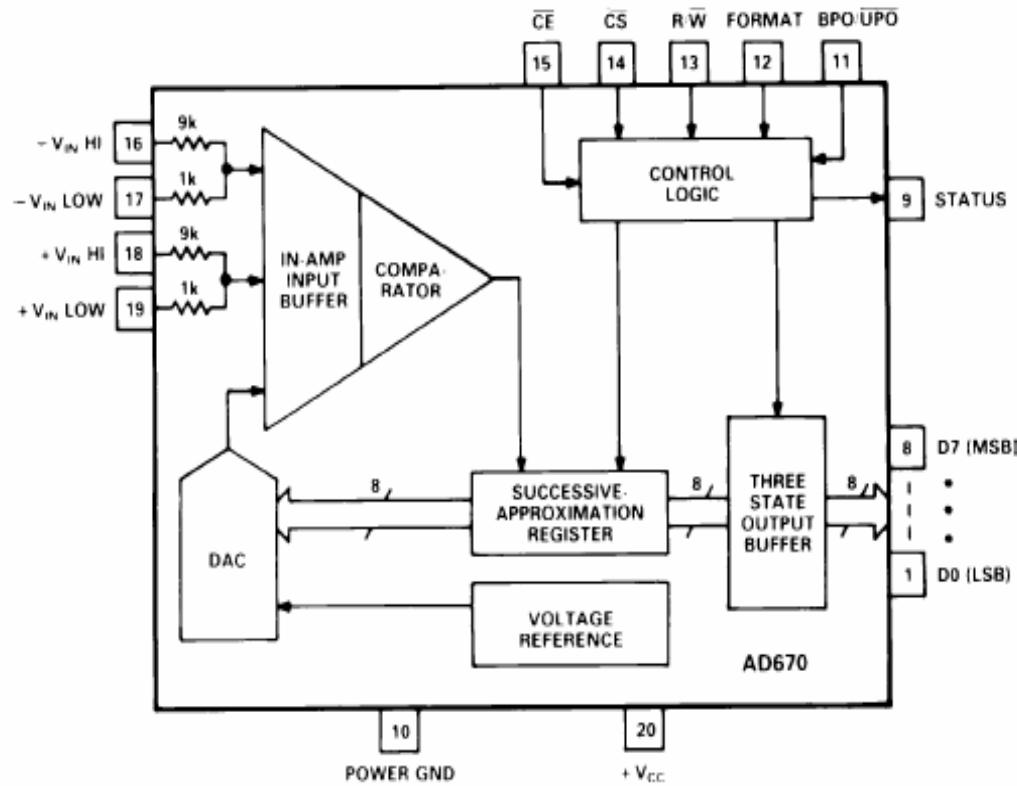


Unipolar (BPO = 0)

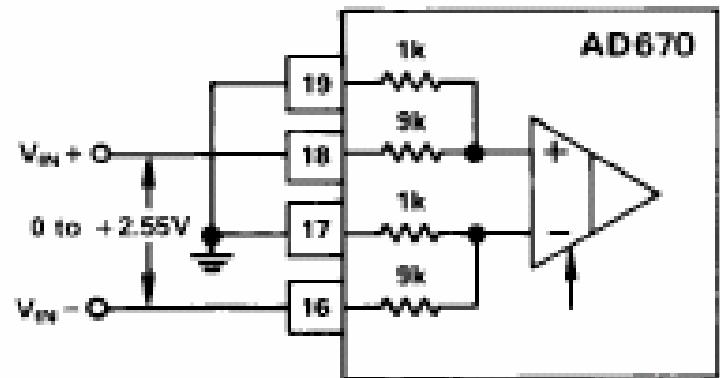


2a. 0 V to 2.55 V (10 mV/LSB)

Bipolar (BPO = 1)

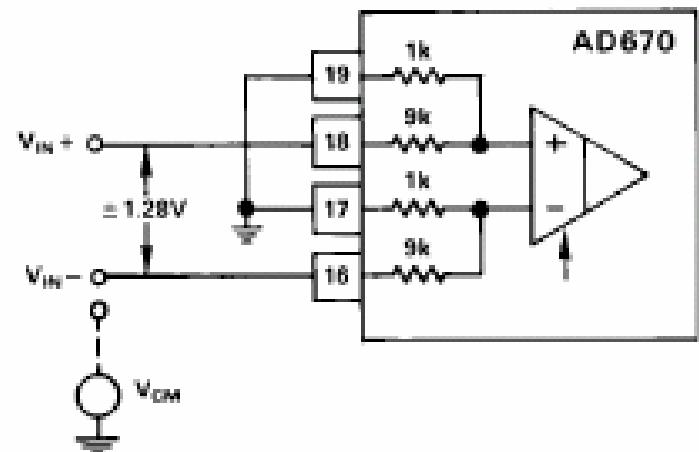

3a. $\pm 1.28 \text{ V Range}$

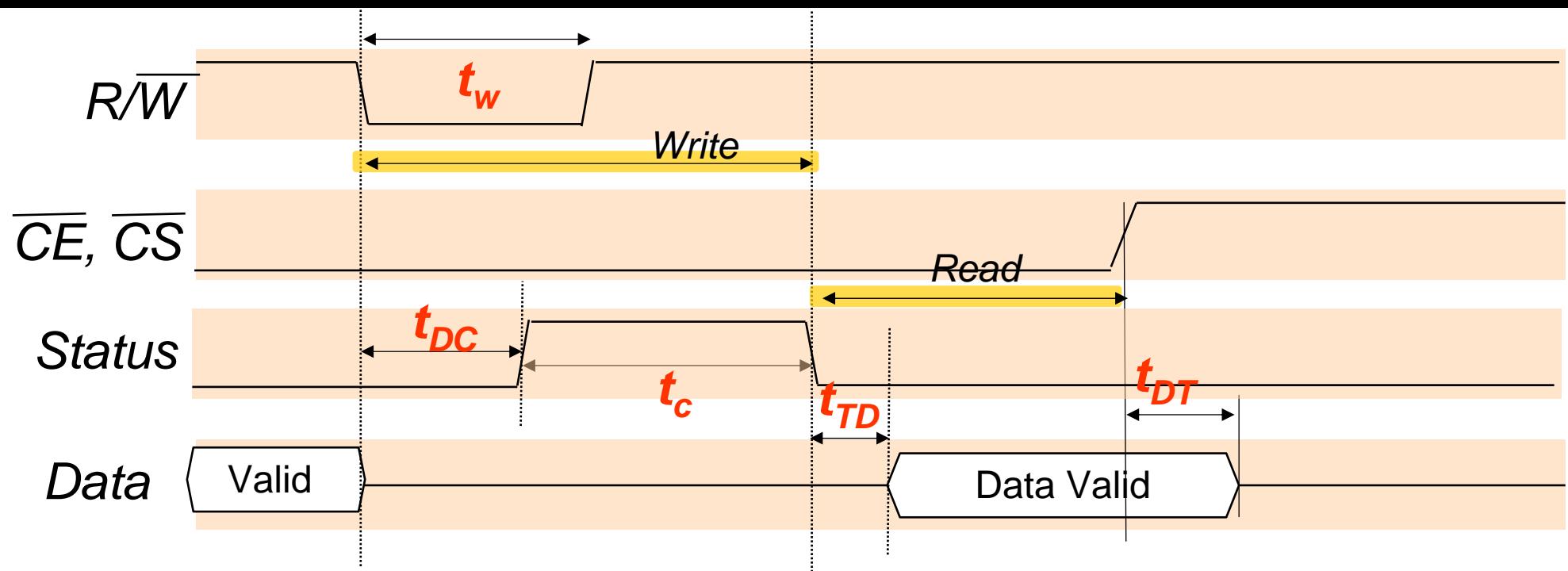Single Write, Single Read Operation (see data sheet for other modes)



t_w (write/start pulse width) = 300ns (min)

t_{DC} (delay to start conversion) = 700ns (max)


t_c (conversion time) = 10 μ s (max)

t_{TD} (Bus Access Time) = 250 (max)

t_{DT} (Output Float Delay) = 150 (max)

- Control bits \overline{CE} and \overline{CS} can be wired to ground if A/D is the only chip driving the bus
- Suggestion: tie \overline{CE} and \overline{CS} pins together and hardwire BPO and Format

Simple A/D Interface FSM

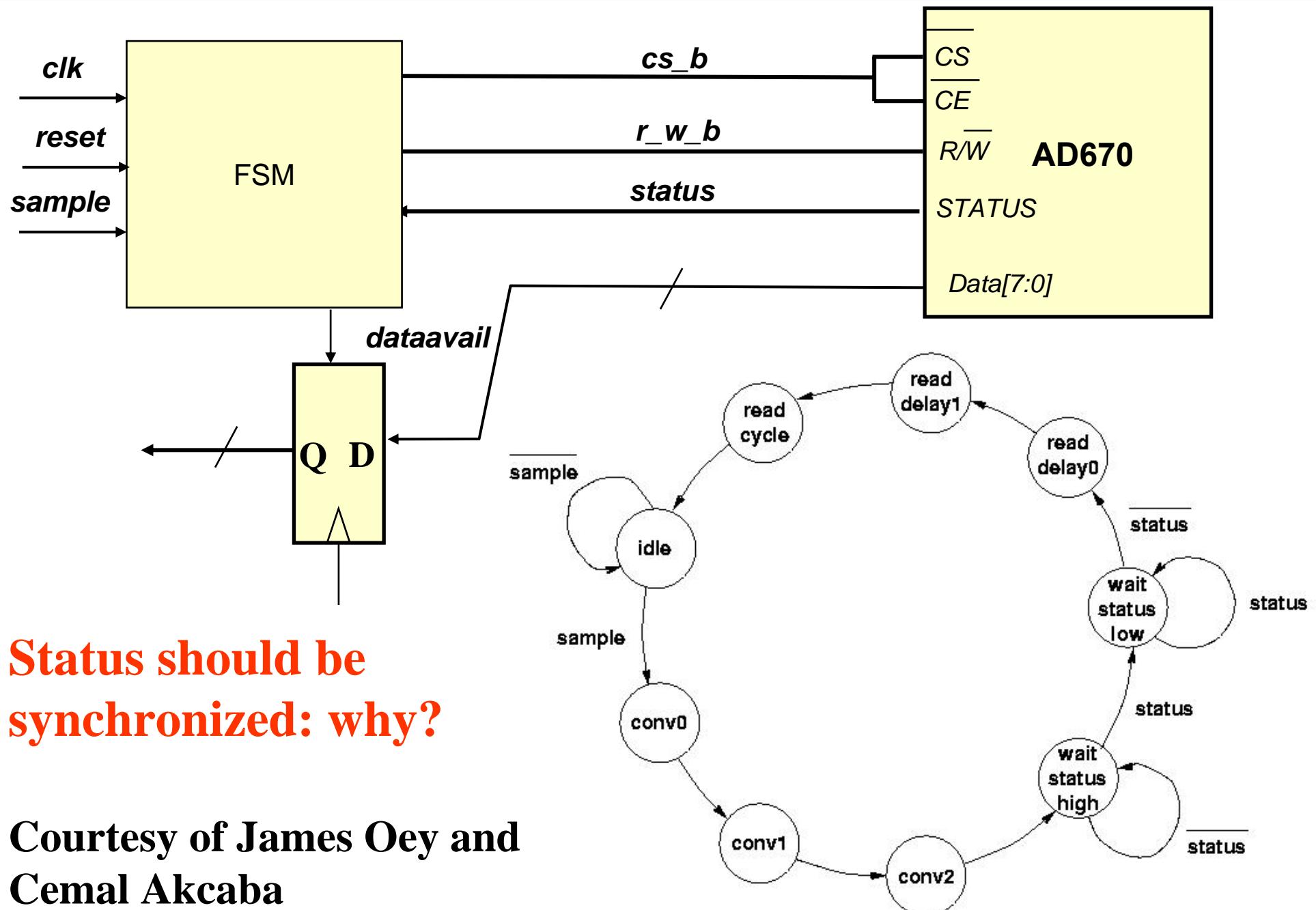

```
module AD670 (clk, reset, sample, dataavail,  
r_wbar, cs_bar, status, state);  
  
// System Clk  
input clk;  
// Global Reset signal, assume it is synchronized  
input reset;  
  
// User Interface  
input sample;  
output dataavail;  
  
// A-D Interface  
input status;  
reg status_d1, status_d2;  
output r_wbar, cs_bar;  
output [3:0] state;  
  
// internal state  
reg [3:0] state;  
reg [3:0] nextstate;  
reg r_wbar_int, r_wbar;  
reg cs_bar_int, cs_bar;  
reg dataavail;
```

1/5

```
// State declarations.  
parameter IDLE = 0;  
parameter CONV0 = 1;  
parameter CONV1 = 2;  
parameter CONV2 = 3;  
parameter WAITSTATUSHIGH = 4;  
parameter WAITSTATUSLOW = 5;  
parameter READDELAY0 = 6;  
parameter READDELAY1 = 7;  
parameter READCYCLE = 8;  
  
always @ (posedge clk or negedge reset)  
begin  
    if (!reset) state <= IDLE;  
    else state <= nextstate;  
  
    status_d1 <= status;  
    status_d2 <= status_d1;  
  
    r_wbar <= r_wbar_int;  
    cs_bar <= cs_bar_int;  
end
```

2/5

```
always @ (state or status_d2 or sample) begin
    // defaults
    r_wbar_int = 1; cs_bar_int = 1; dataavail = 0;

    case (state)

        IDLE: begin
            if(sample) nextstate = CONV0;
            else nextstate = IDLE;
            end

        CONV0:
        begin
            r_wbar_int = 0;
            cs_bar_int = 0;
            nextstate = CONV1;
            end

        CONV1:
        begin
            r_wbar_int = 0;
            cs_bar_int = 0;
            nextstate = CONV2;
            end
    endcase
end
```

3/5

```
CONV2:
begin
    r_wbar_int = 0;
    cs_bar_int = 0;
    nextstate = WAITSTATUSHIGH;
end

WAITSTATUSHIGH:
begin
    cs_bar_int = 0;
    if (status_d2) nextstate = WAITSTATUSLOW;
    else nextstate = WAITSTATUSHIGH;
end

WAITSTATUSLOW:
begin
    cs_bar_int = 0;
    if (!status_d2) nextstate = READDELAY0;
    else nextstate = WAITSTATUSLOW;
end
```

4/5


```
READDELAY0:  
begin  
    cs_bar_int = 0;  
    nextstate = READDELAY1;  
end  
  
READDELAY1:  
begin  
    cs_bar_int = 0;  
    nextstate = READCYCLE;  
end  
  
READCYCLE:  
begin  
    cs_bar_int = 0;  
    dataavail = 1;  
    nextstate = IDLE;  
end  
  
    default: nextstate = IDLE;  
endcase // case(state)  
end // always @ (state or status_d2 or sample)  
endmodule // adcInterface
```

5/5

Simulation


On reset, present state goes to 0

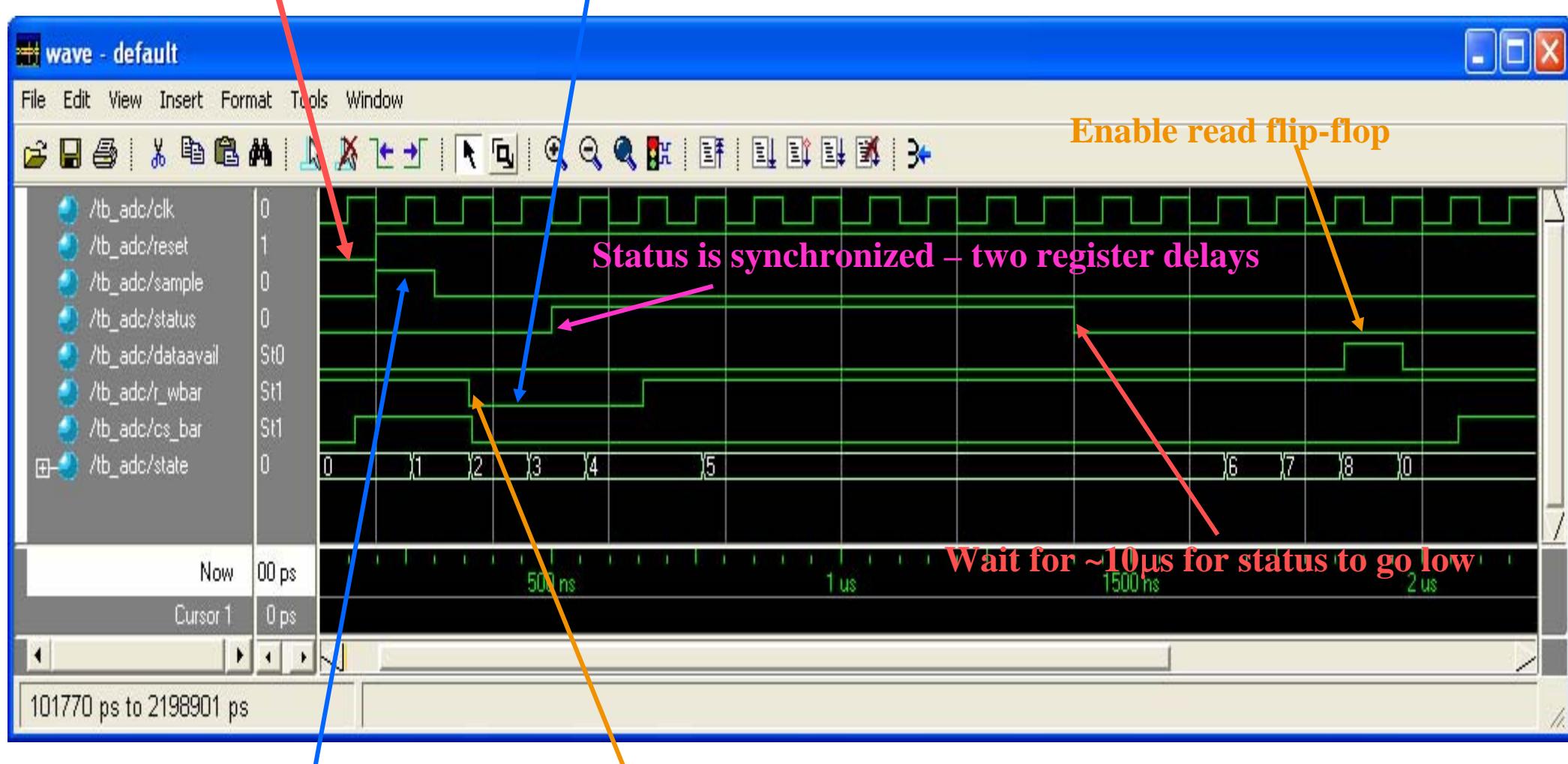r_w_b must stay low for at least 3 cycles (@ 100ns period)





Sample pulse initiates
data conversion

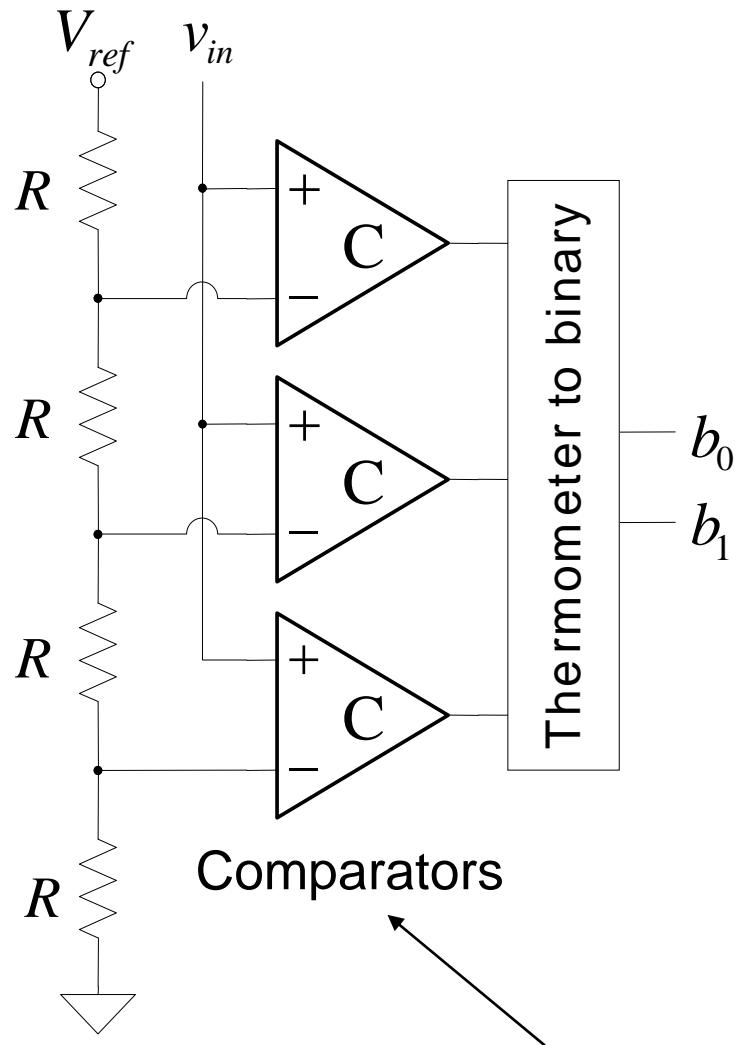Notice a one cycle delay since A/D
control signal delayed through a register



- Brute-force A/D conversion
- Simultaneously compare the analog value with every possible reference value
- Fastest method of A/D conversion
- Size scales exponentially with precision
(requires 2^N comparators)

Can be implemented as OpAmp in open loop

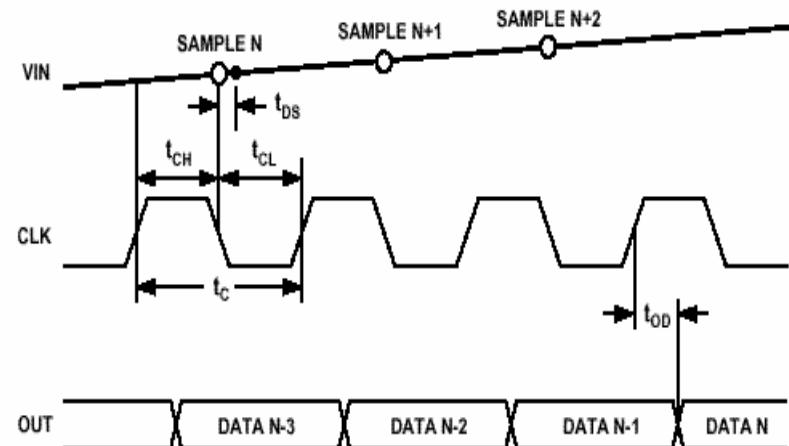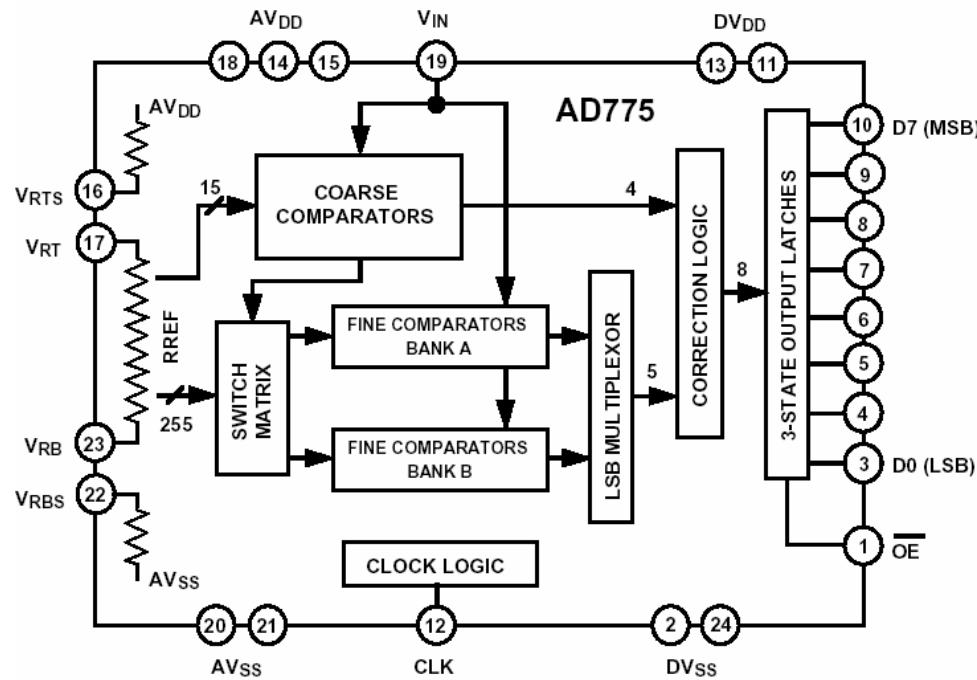


TIMING SPECIFICATIONS


	Symbol	Min	Typ	Max	Units
Maximum Conversion Rate		20	35		MHz
Clock Period	t _C	50			ns
Clock High	t _{CH}	25			ns
Clock Low	t _{CL}	25			ns
Output Delay	t _{OD}		18	30	ns
Pipeline Delay (Latency)				2.5	Clock Cycles
Sampling Delay	t _{DS}		4		ns
Aperture Jitter			30		ps

High Performance Converters: Use Pipelining and Parallelism!

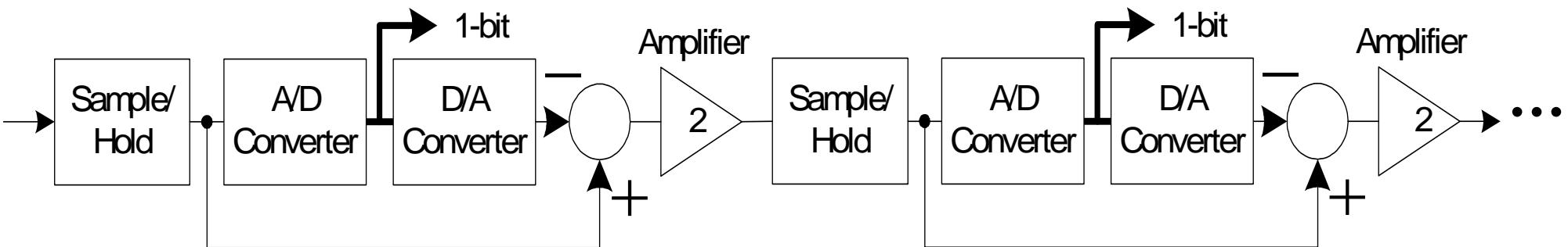Pipelining (used in video rate, RF basestations, etc.)



Parallelism (use many slower A/D's in parallel to build very high speed A/D converters)

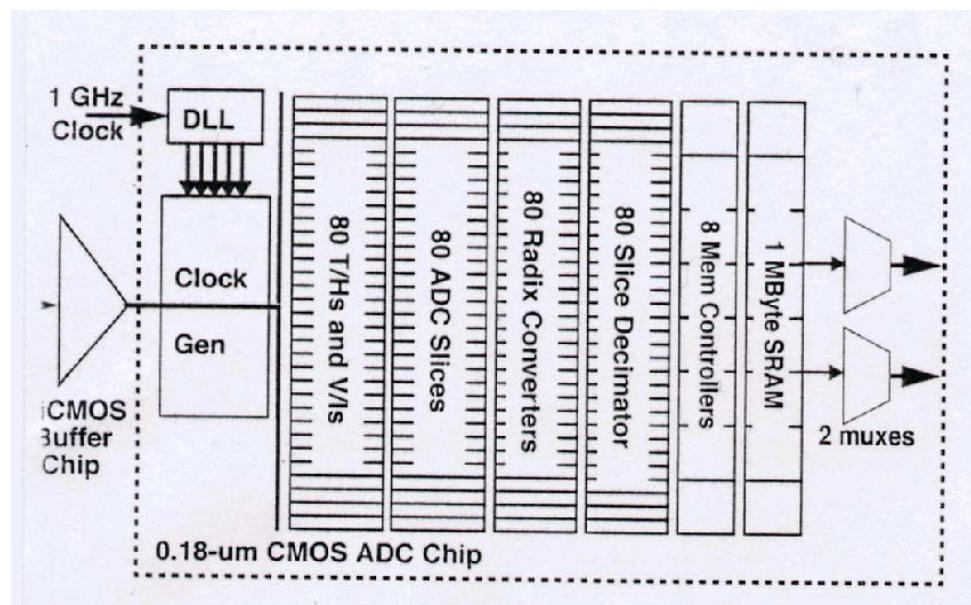

[ISSCC 2003],
Poulton et. al.

20Gsamp/sec,
8-bit ADC
from Agilent Labs

- Analog blocks are integral components of any system. Need data converters (analog to digital and digital to analog), analog processing (OpAmps circuits, switched capacitors filters, etc.), power converters (e.g., DC-DC conversion), etc.
- We looked at example interfaces for A/D and D/A converters
 - Make sure you register critical signals (enables, R/W, etc.)
- **Analog design incorporate digital principles**
 - Glitch free operation using coding
 - Parallelism and Pipelining!
 - More advanced concepts such as calibration