 



# L15: VLSI Integration and Performance Transformations





## Acknowledgement:

Lecture material adapted from J. Rabaey, A. Chandrakasan, B. Nikolic, “Digital Integrated Circuits: A Design Perspective” Copyright 2003 Prentice Hall/Pearson.

Curt Schurgers

 


In 1965, Gordon Moore was preparing a speech and made a memorable observation. When he started to graph data about the growth in memory chip performance, he realized there was a striking trend. Each new chip contained roughly twice as much capacity as its predecessor, and each chip was released within 18-24 months of the previous chip. If this trend continued, he reasoned, computing power would rise exponentially over relatively brief periods of time.

 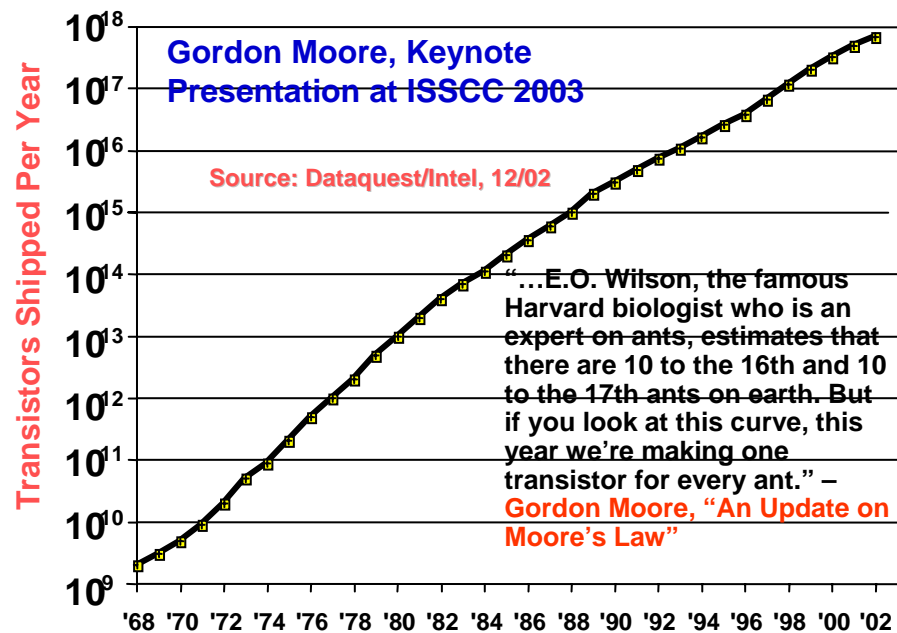

Courtesy of S. Borkar (Intel)



## 3-D Cross-Section

 

**N-channel MOSFET**


**P-channel MOSFET**

## Circuit Representation

 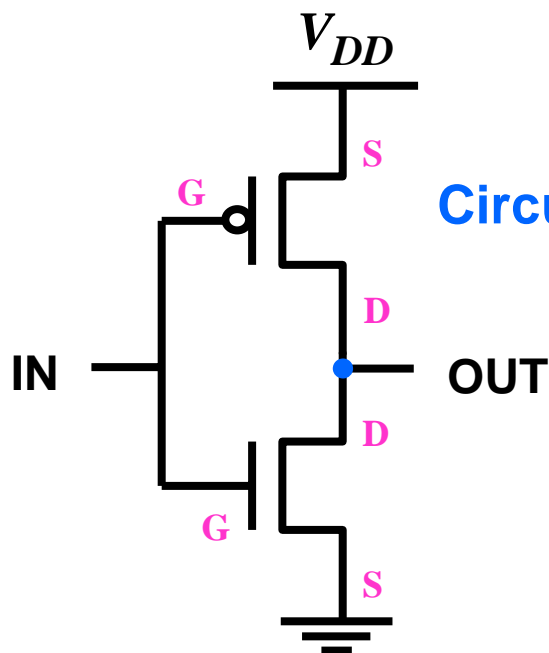

 
## Layout


- Follow simple design rules (contract between process and circuit designers)



 Itanium has 6 integer execution units like this




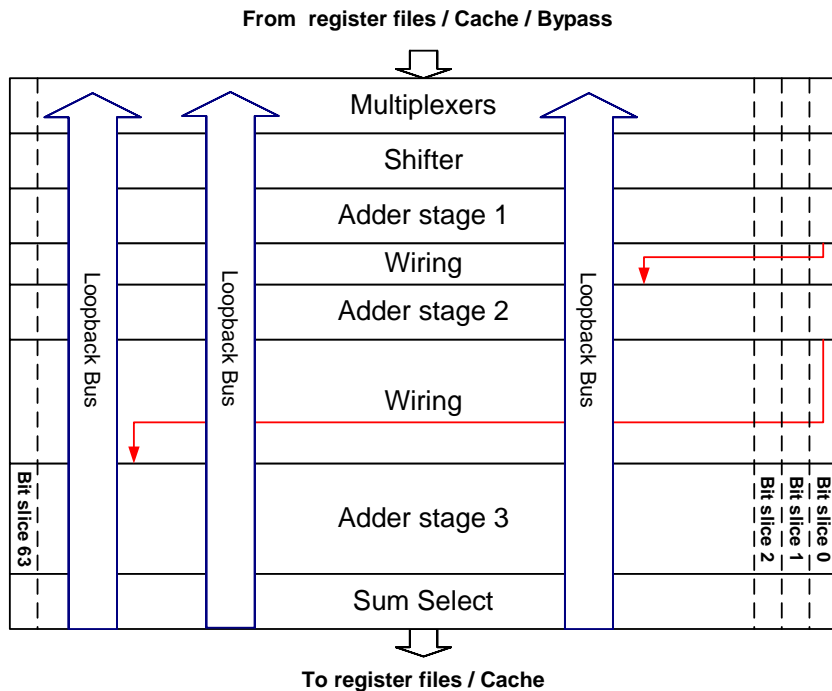Die photograph of the Itanium integer datapath




Bit-slice Design Methodology

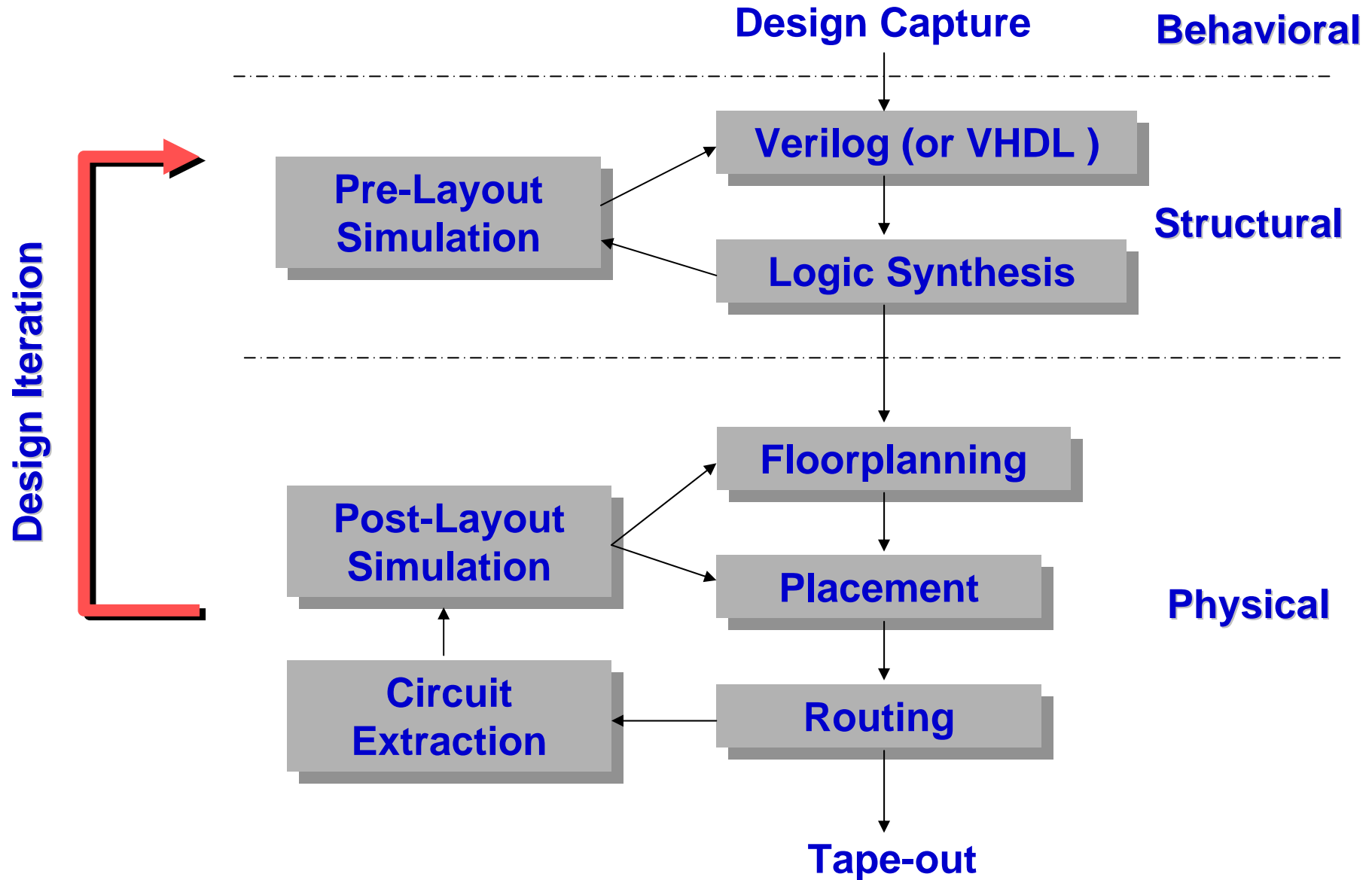- Hand crafting the layout to achieve maximum clock rates (> 1Ghz)
- Exploits regularity in datapath structure to optimize interconnects



 **Most Common Design Approach for Designs up to 500Mhz  
Clock Rates**



**Power Supply Line ( $V_{DD}$ )**      **Delay in (ns)!!**


Path	1.2V - 125°C	1.6V - 40°C
$In1-t_{pLH}$	$0.073+7.98C+0.317T$	$0.020+2.73C+0.253T$
$In1-t_{pHL}$	$0.069+8.43C+0.364T$	$0.018+2.14C+0.292T$
$In2-t_{pLH}$	$0.101+7.97C+0.318T$	$0.026+2.38C+0.255T$
$In2-t_{pHL}$	$0.097+8.42C+0.325T$	$0.023+2.14C+0.269T$
$In3-t_{pLH}$	$0.120+8.00C+0.318T$	$0.031+2.37C+0.258T$
$In3-t_{pHL}$	$0.110+8.41C+0.280T$	$0.027+2.15C+0.223T$

3-input NAND cell  
 (from ST Microelectronics):  
 $C$  = Load capacitance  
 $T$  = input rise/fall time


**Ground Supply Line (GND)**

- Each library cell (FF, NAND, NOR, INV, etc.) and the variations on size (strength of the gate) is fully characterized across temperature, loading, etc.

## 2-level metal technology

 

## Current Day Technology

 


*Cell-structure hidden under interconnect layers*

- With limited interconnect layers, dedicated routing channels between rows of standard cells are needed
- Width of the cell allowed to vary to accommodate complexity
- **Interconnect plays a significant role in speed of a digital circuit**



# Verilog to ASIC Layout (the push button approach)

```
module adder64 (a, b, sum);  
  input [63:0] a, b;  
  output [63:0] sum;  
  
  assign sum = a + b;  
endmodule
```

After  
Synthesis

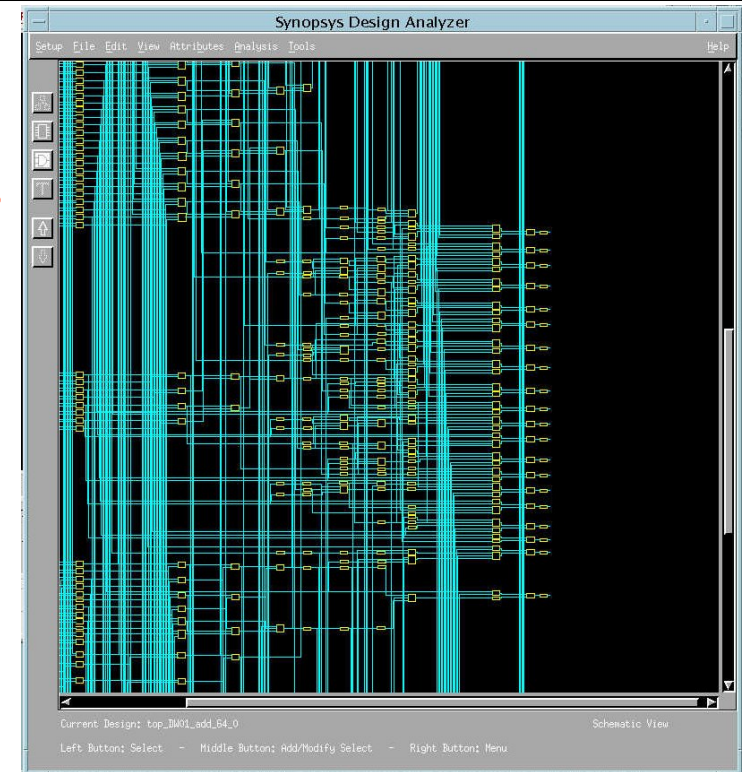


After Routing

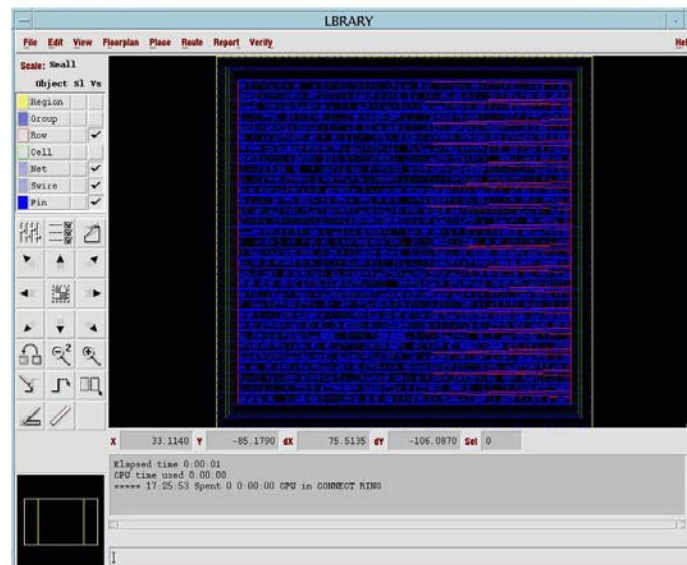 

After  
Placement




 
## 256×32 (or 8192 bit) SRAM Generated by hard-macro module generator



- Generate highly regular structures (entire memories, multipliers, etc.) with **a few lines of code**
- Verilog models for memories **automatically** generated based on size


## Clock skew, courtesy Alpha

  



For 1Ghz clock, skew budget is 100ps.  
 Variations along different paths arise from:

- Device:  $V_T$ ,  $W/L$ , etc.
- Environment:  $V_{DD}$ ,  $^{\circ}C$
- Interconnect: dielectric thickness variation

## IBM Clock Routing

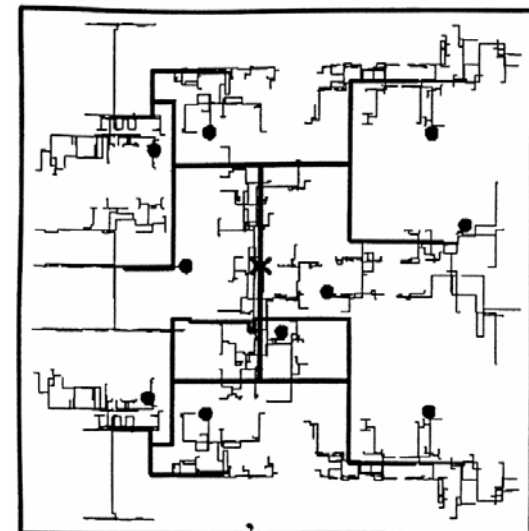
  
# Analog Circuits: Clock Frequency Multiplication (Phase Locked Loop)




Intel 486, 50Mhz

- VCO → produces high frequency square wave
- Divider → divides down VCO frequency
- PFD → compares phase of ref and div
- Loop filter → extracts phase error information


**Used widely in digital systems for clock synthesis  
(a standard IP block in most ASIC flows)**

Courtesy M. Perrott

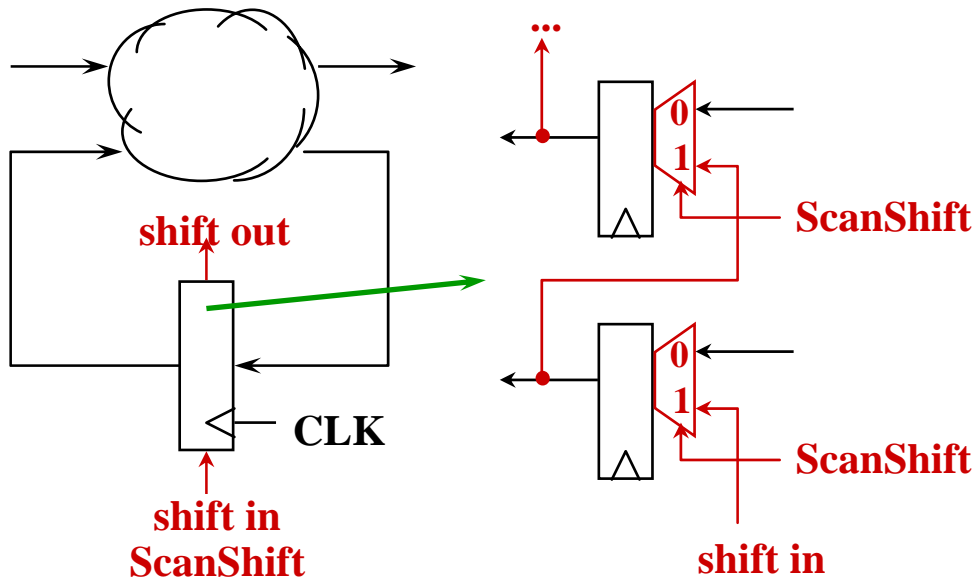

**Idea:** have a mode in which all registers are chained into one giant shift register which can be loaded/read-out bit serially. Test remaining (combinational) logic by

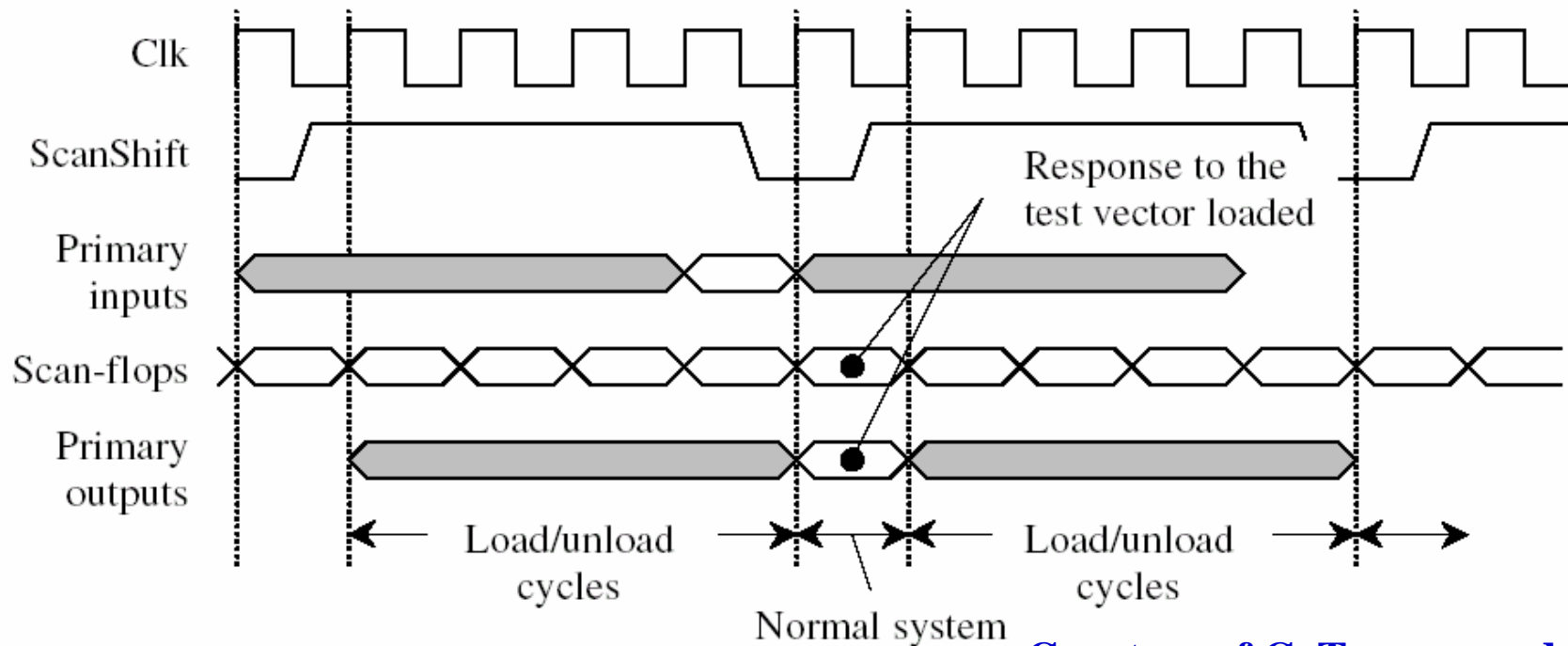- (1) in “test” mode, shift in new values for all register bits thus setting up the inputs to the combinational logic
- (2) clock the circuit once in “normal” mode, latching the outputs of the combinational logic back into the registers
- (3) in “test” mode, shift out the values of all register bits and compare against expected results.




Courtesy of C. Terman and IEEE Press

- There are a large number of implementations of the same functionality
- These implementations present a different point in the area-time-power design space
- Behavioral transformations allow exploring the design space a high-level

## Optimization metrics:

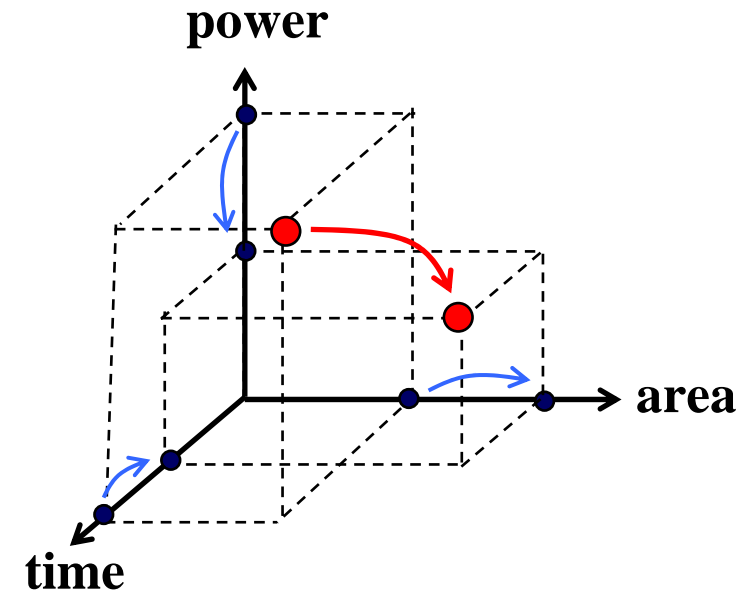1. **Area** of the design
2. **Throughput** or sample time  $T_S$
3. **Latency**: clock cycles between the input and associated output change
4. **Power** consumption
5. **Energy** of executing a task
6. ...



## Conventional Multiplication

$$Z = X \cdot Y$$


				$X_3$	$X_2$	$X_1$	$X_0$
				$Y_3$	$Y_2$	$Y_1$	$Y_0$
				$X_3 \cdot Y_0$	$X_2 \cdot Y_0$	$X_1 \cdot Y_0$	$X_0 \cdot Y_0$
			$X_3 \cdot Y_1$	$X_2 \cdot Y_1$	$X_1 \cdot Y_1$	$X_0 \cdot Y_1$	
		$X_3 \cdot Y_2$	$X_2 \cdot Y_2$	$X_1 \cdot Y_2$	$X_0 \cdot Y_2$		
	$X_3 \cdot Y_3$	$X_2 \cdot Y_3$	$X_1 \cdot Y_3$	$X_0 \cdot Y_3$			
$Z_7$	$Z_6$	$Z_5$	$Z_4$	$Z_3$	$Z_2$	$Z_1$	$Z_0$

## Constant multiplication (become hardwired shifts and adds)

$$Z = X \cdot (1001)_2$$


				$X_3$	$X_2$	$X_1$	$X_0$
				$1$	$0$	$0$	$1$
				$X_3$	$X_2$	$X_1$	$X_0$
	$X_3$	$X_2$	$X_1$	$X_0$			
$Z_7$	$Z_6$	$Z_5$	$Z_4$	$Z_3$	$Z_2$	$Z_1$	$Z_0$

$$Y = (1001)_2 = 2^3 + 2^0$$

 



Canonical signed digit representation is used to increase the number of zeros. It uses digits  $\{-1, 0, 1\}$  instead of only  $\{0, 1\}$ .

 Iterative encoding: replace string of consecutive 1's




Worst case CSD has 50% non zero bits

01101111

  


||

1001̄0001̄

 


Shift translates to re-wiring

## Commutativity

 


$$A + B = B + A$$

## Distributivity

 


$$(A + B) C = AB + BC$$

## Associativity

 


$$(A + B) + C = A + (B + C)$$


## Common sub-expressions

 




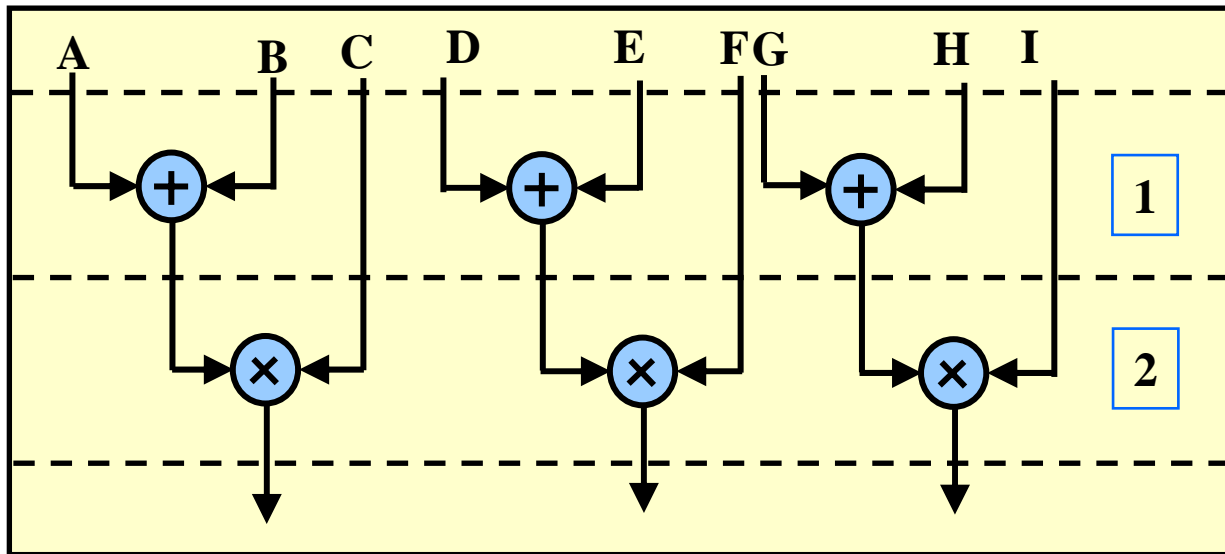

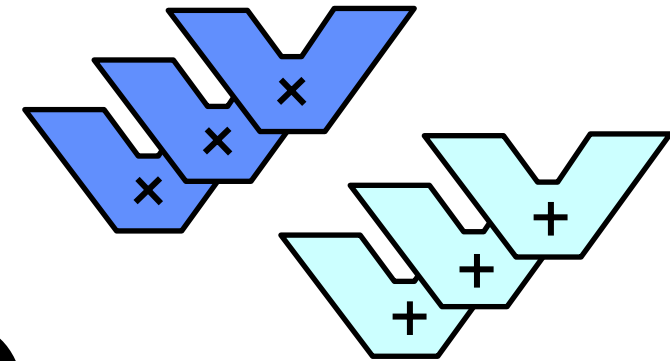
**Time multiplexing: mapped to 3 multipliers and 3 adders**



*distributivity*

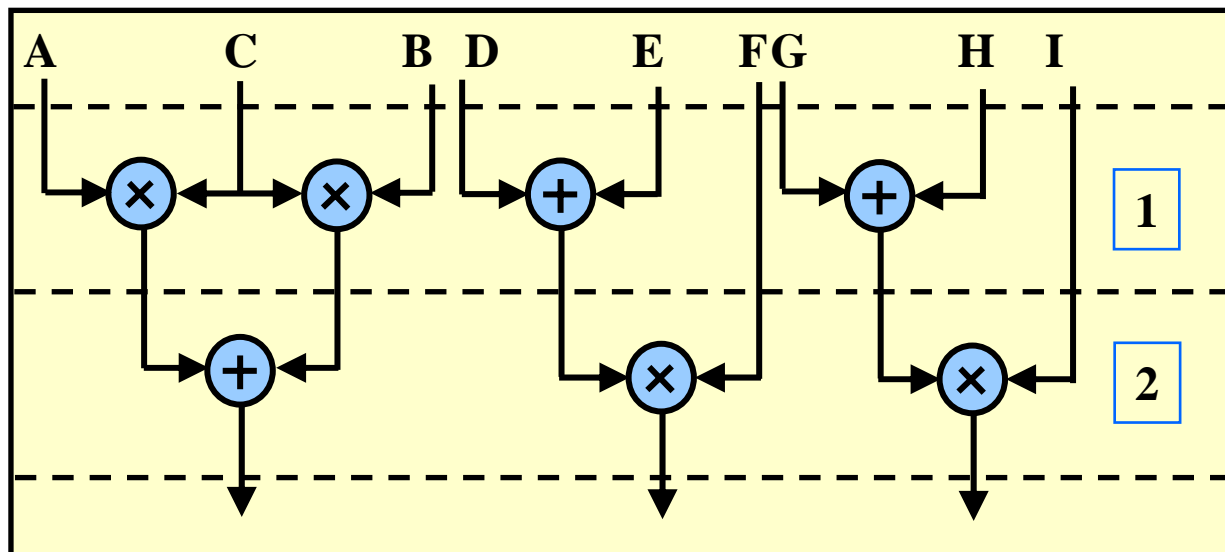


 **Reduce number of operators to 2 multipliers and 2 adders**




 **Retiming is the action of moving delay around in the systems**

- Delays have to be moved from ALL inputs to ALL outputs or vice versa



 **Cutset retiming:** A cutset intersects the edges, such that this would result in two disjoint partitions of these edges being cut. To retime, delays are moved from the ingoing to the outgoing edges or vice versa.







**Benefits of retiming:**

- Modify critical path delay
- Reduce total number of registers

Retiming Synchronous Circuitry

 
Charles E. Leiserson and James B. Saxe  
August 20, 1986.



 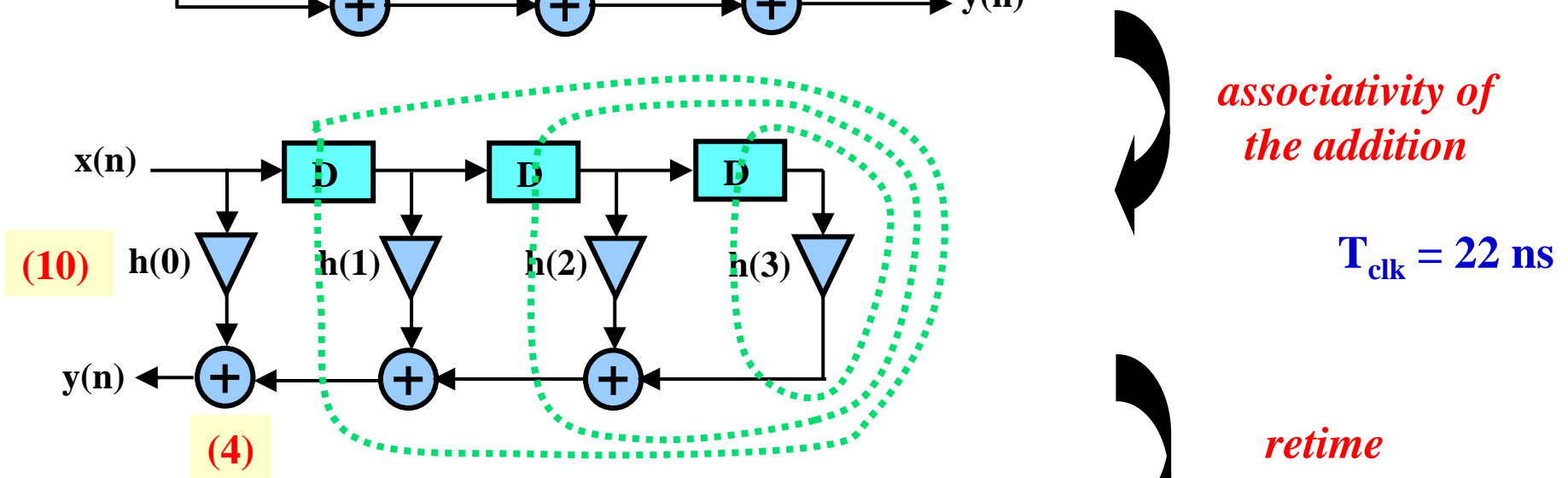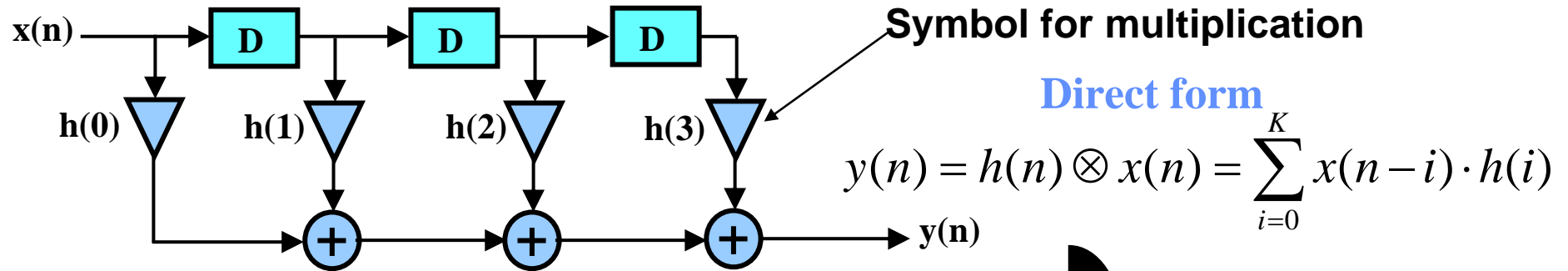


**Note:** here we use a first cut analysis that assumes the delay of a chain of operators is the sum of their individual delays. This is not accurate.
 
# Pipelining, Just Another Transformation (**Pipelining = Adding Delays + Retiming**)




Contrary to retiming,  
pipelining adds extra registers  
to the system

*add input  
registers*

 


*retime*

 

How to pipeline:


1. Add extra registers at *all* inputs
2. Retime

$$y(n) = x(n) + A y(n-1)$$

 


Try pipelining this structure

How about pipelining this structure!

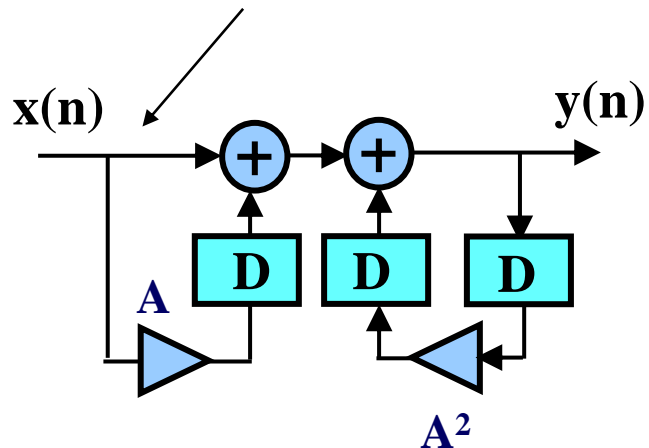


loop unrolling

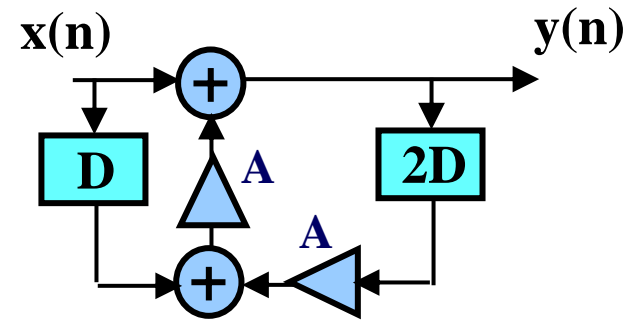


$$y(n) = x(n) + A[x(n-1) + A y(n-2)]$$

distributivity


 


associativity

 


precomputed



retiming

  

Temp Variation & Hot spots

 


  **With 100b transistors, 1b unusable (variations)**



**Deterministic design techniques inadequate in the future**
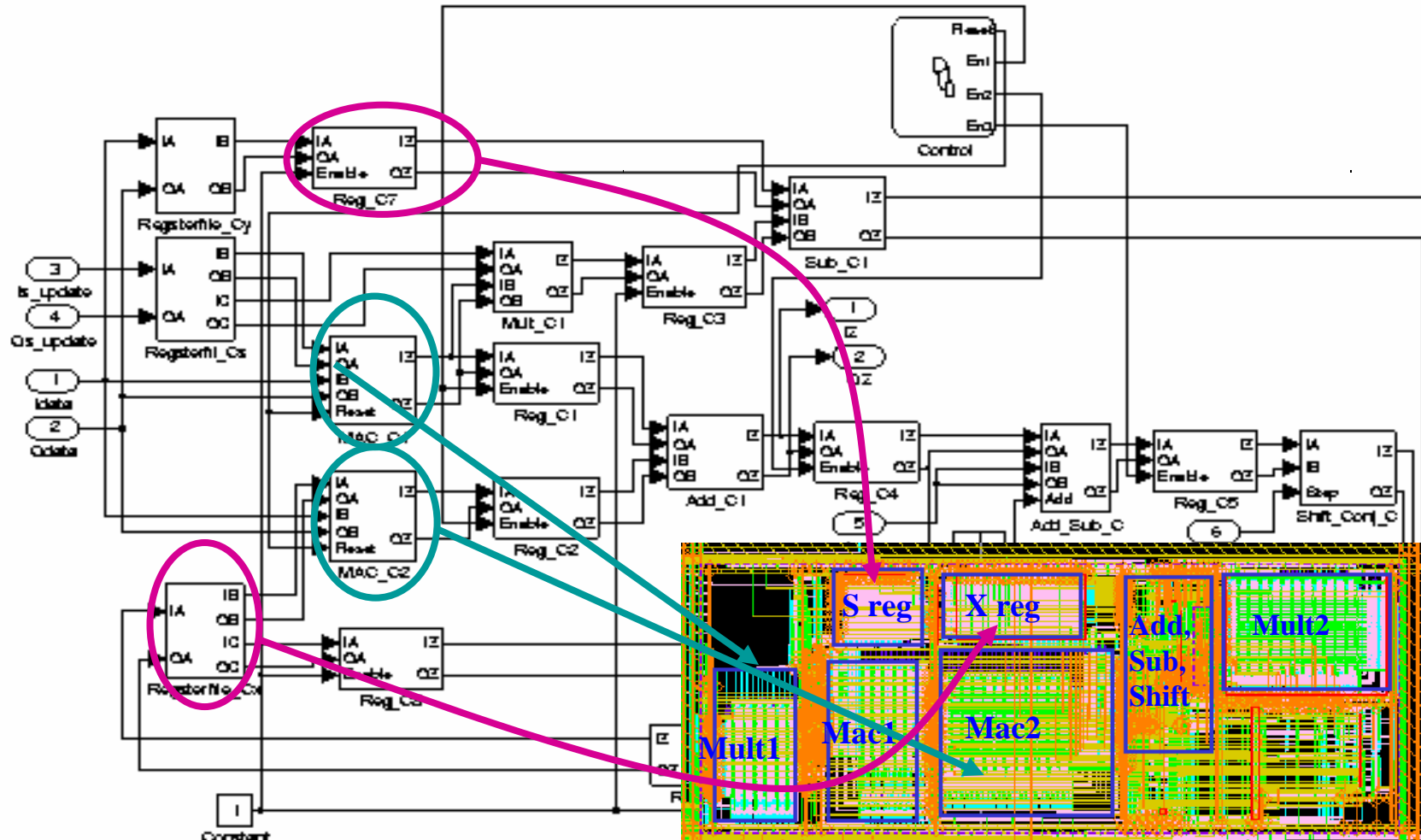
# Trends: "Chip in a Day" (Matlab/Simulink to Silicon...)




**Map algorithms directly to silicon - bypass writing Verilog!**

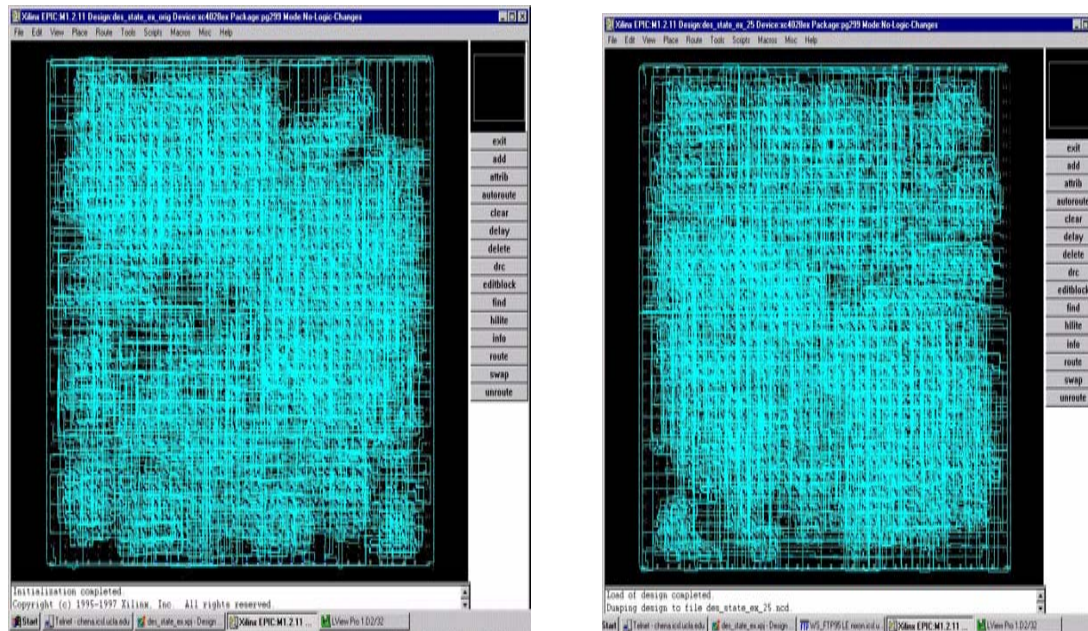**Courtesy of R. Brodersen**

**Fingerprinting** is a technique to deter people from illegally redistributing legally obtained IP by enabling the author of the IP to uniquely identify the original buyer of the resold copy.

The essence of the **watermarking** approach is to encode the author's signature. The selection, encoding, and embedding of the signature must result in minimal performance and storage overhead.



*same functionality, same area, same performance  
watermark of 4768 bits embedded  
(courtesy of G. Qu, M. Potkonjak)*