


# L4: Sequential Building Blocks

## (Flip-flops, Latches and Registers)



 
### Acknowledgements:

- Lecture material adapted from R. Katz, G. Borriello, “Contemporary Logic Design” (second edition), Prentice-Hall/Pearson Education, 2005.
- Lecture material adapted from J. Rabaey, A. Chandrakasan, B. Nikolic, “Digital Integrated Circuits: A Design Perspective” Copyright 2003 Prentice Hall/Pearson.




 - **Combinational logic circuits are memoryless**
- **No feedback in combinational logic circuits**
- **Output assumes the function implemented by the logic network, assuming that the switching transients have settled**
- **Outputs can have multiple logical transitions before settling to the correct value**








- **Sequential circuits have memory (i.e., remember the past)**
- **The current state is “held” in memory and the next state is computed based the current state and the current inputs**
- **In a synchronous systems, the **clock signal** orchestrates the sequence of events**


## Adding N inputs (N-1 Adders)

 

## Using a sequential (serial) approach


 


 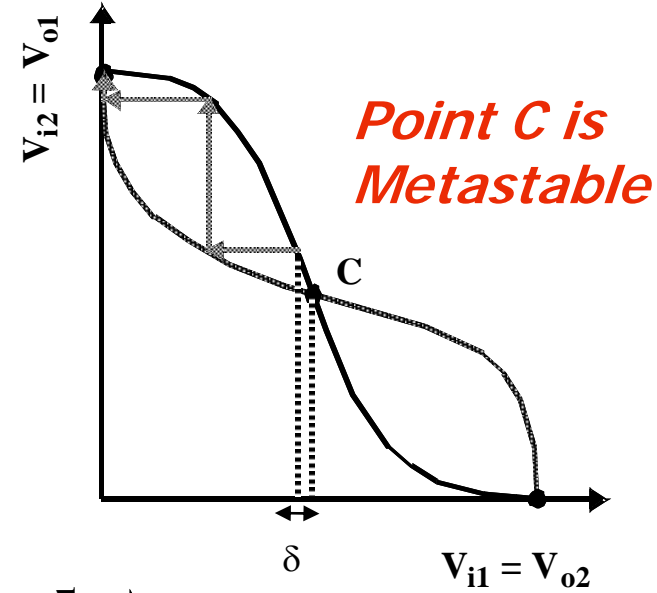  

 


$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q$	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State

  


- Flip-flop refers to a bi-stable element (edge-triggered registers are also called flip-flops) – this circuit is not clocked and outputs change “asynchronously” with the inputs
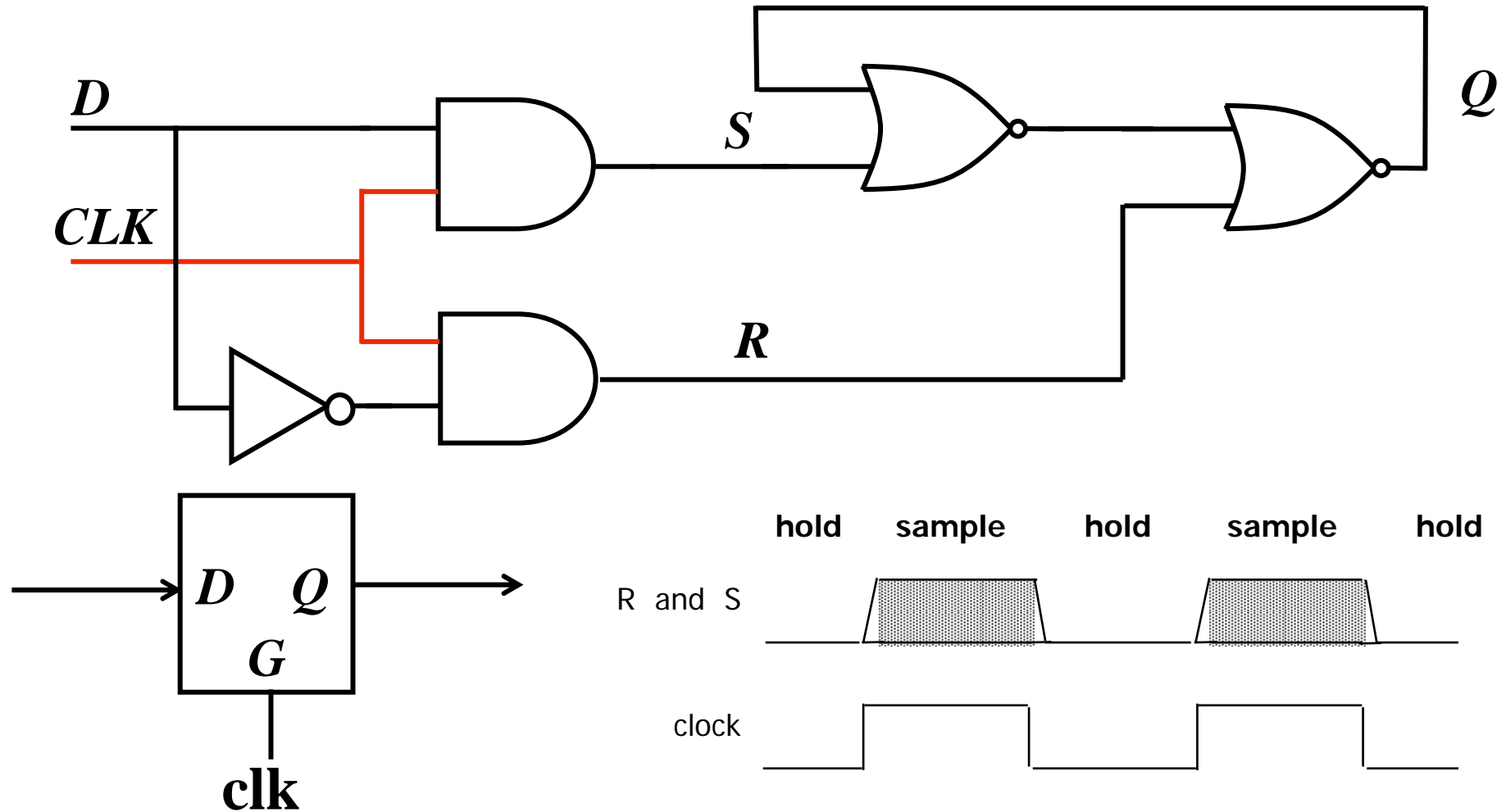
# Making a Clocked Memory Element: Positive D-Latch




- **A Positive D-Latch:** Passes input  $D$  to output  $Q$  when  $CLK$  is high and holds state when clock is low (i.e., ignores input  $D$ )
- **A Latch is level-sensitive:** invert clock for a negative latch



### 2:1 multiplexor

 


### Positive Latch

 


### Negative Latch

  



 

OPERATING MODES	INPUTS		OUTPUTS	
	LE <sub>n-n</sub>	nD	nQ	n $\bar{Q}$
data enabled	H	L	L	H
	H	H	H	L
data latched	L	X	q	$\bar{q}$

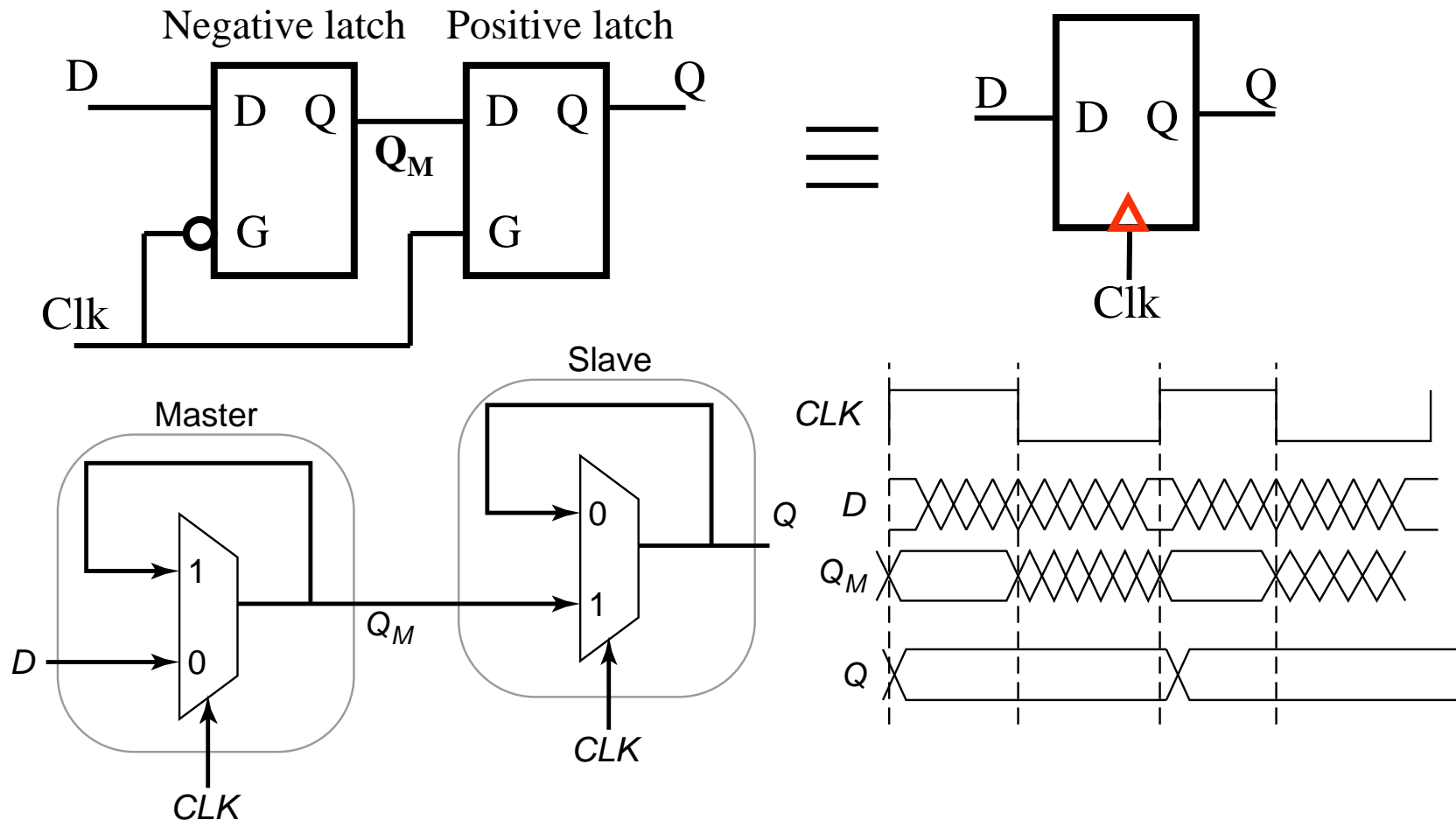

## ■ Master-Slave Register

- Use negative clock phase to latch inputs into first latch
- Use positive clock to change outputs with second latch


## ■ View pair as one basic unit

- master-slave flip-flop twice as much logic



*Edge triggered device sample inputs on the event edge*

*Transparent latches sample inputs as long as the clock is asserted*


Timing Diagram:

 

  *Behavior the same unless input changes while the clock is high*



 **Bubble here for negative edge triggered register**



***Clock:***

Periodic Event, causes state of memory element to change

memory element can be updated on the: rising edge, falling edge, high level, low level

***Setup Time ( $T_{su}$ )***

Minimum time before the clocking event by which the input must be stable

***Hold Time ( $T_h$ )***



Minimum time after the clocking event during which the input must remain stable

***Propagation Delay ( $T_{cq}$  for an edge-triggered register and  $T_{dq}$  for a latch)***

Delay overhead of the memory element

There is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized
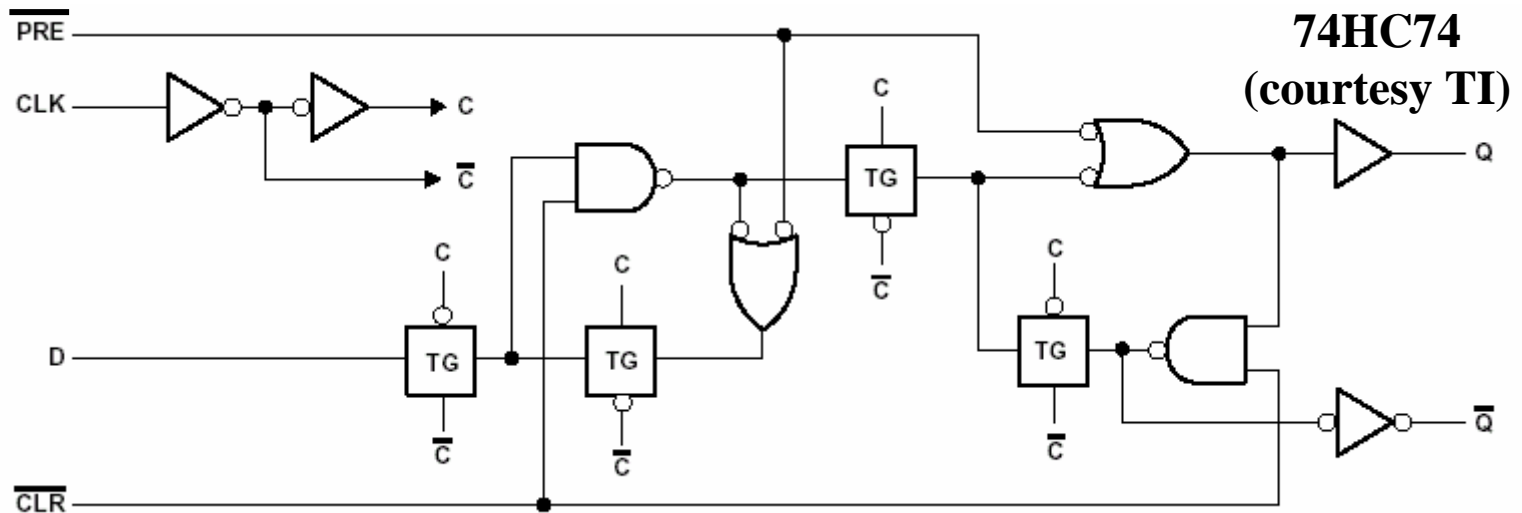 
# 74HC74 (Positive Edge-Triggered Register)





FUNCTION TABLE

INPUTS				OUTPUTS	
PRE	CLR	CLK	D	Q	Q̄
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H↑	H↑
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q <sub>0</sub>	Q̄ <sub>0</sub>

## D-FF with preset and clear

		V <sub>CC</sub>	T <sub>A</sub> = 25°C		SN54HC74		SN74HC74		UNIT
			MIN	MAX	MIN	MAX	MIN	MAX	
f <sub>clock</sub>	Clock frequency	2 V	0	6	0	4.2	0	5	MHz
		4.5 V	0	31	0	21	0	25	
		6 V	0	36	0	25	0	29	
t <sub>w</sub>	Pulse duration	PRE or CLR low	2 V	100	150	125	ns		
			4.5 V	20	30	25			
		CLK high or low	2 V	80	120	100			
			4.5 V	16	24	20			
t <sub>su</sub>	Setup time before CLK↑	Data	2 V	100	150	125	ns		
			4.5 V	20	30	25			
		6 V	17	25	21				
		PRE or CLR inactive	2 V	25	40	30			
			4.5 V	5	8	6			
			6 V	4	7	5			
t <sub>h</sub>	Hold time, data after CLK↑	2 V	0	0	0	ns			
		4.5 V	0	0	0				
		6 V	0	0	0				


 
 


J	K	Q+	$\overline{Q}_+$
0	0	Q	$\overline{Q}$
0	1	0	1
1	0	1	0
1	1	$\overline{Q}$	Q




- Eliminate the forbidden state of the SR Flip-flop
- Use output feedback to guarantee that R and S are never both one

Sample inputs while clock high


Sample inputs while clock low

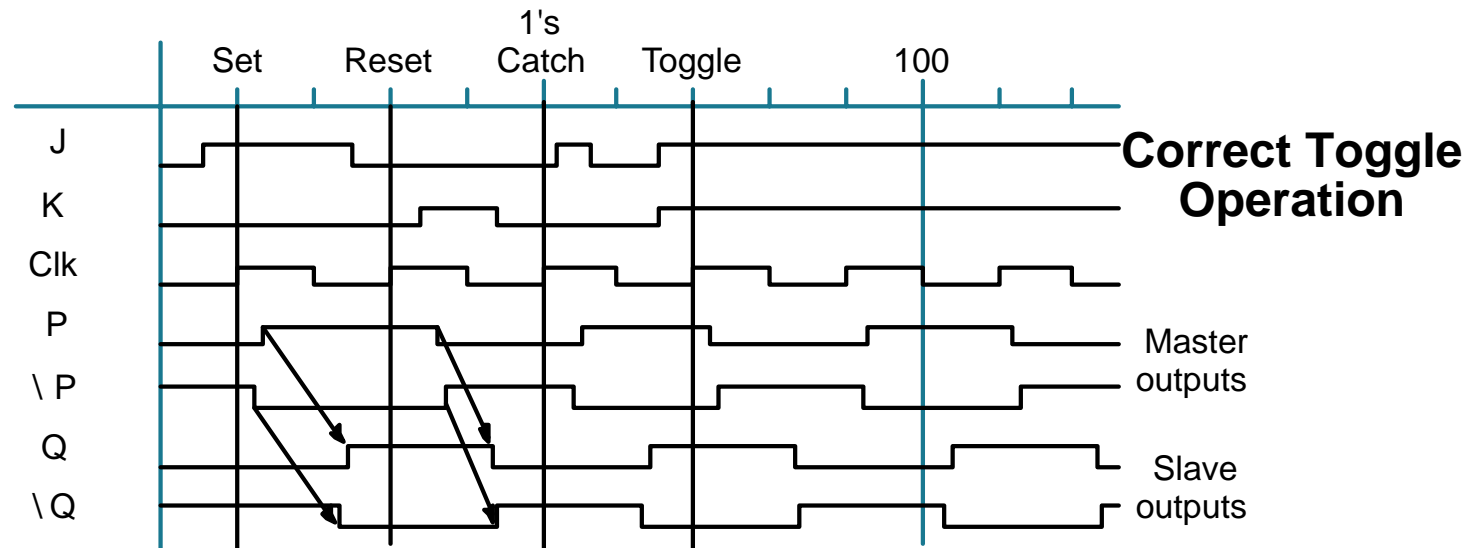 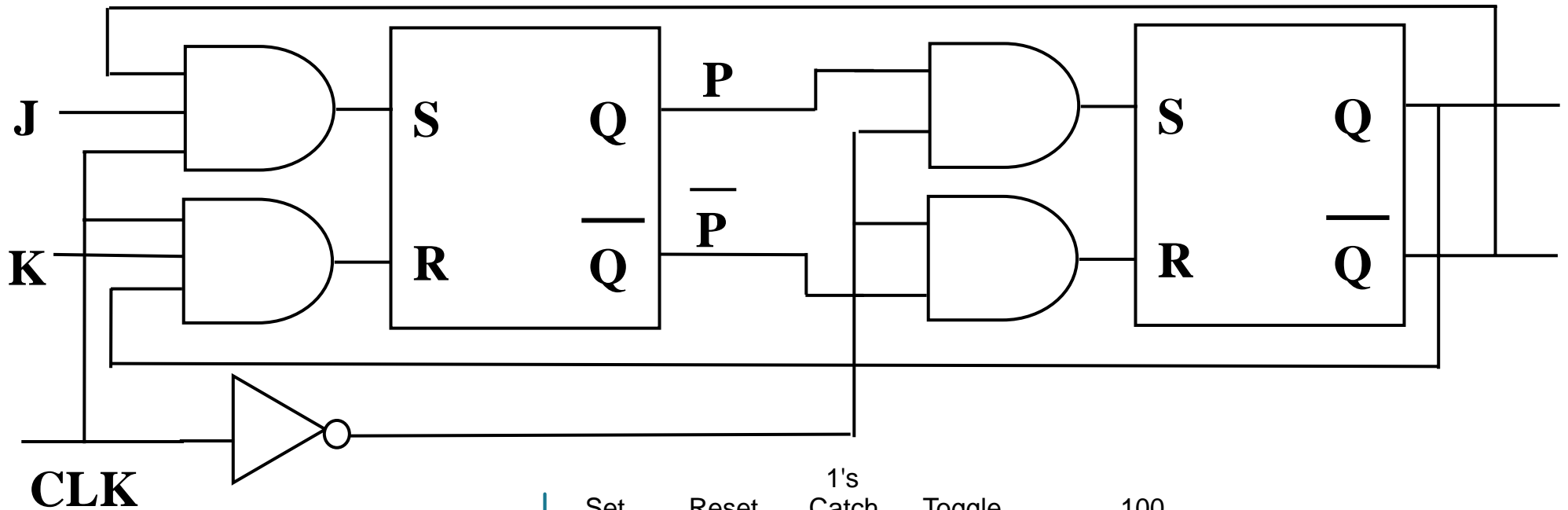

   **Is there a problem with this circuit?**




JK Register Schematic

 




Ways to design an edge-triggered sequential cell:

## Master-Slave Latches

 


## Pulse-Based Register

 


 **Short pulse around clock edge**



- **Pulse registers are widely used in high-performance microprocessor chips (Sun Microsystems, AMD, Intel, etc.)**
- **The can have a negative setup time!**



D	$Q_N$
0	0
1	1

 

T	$Q_N$
0	$Q_{N-1}$
1	$\overline{Q_{N-1}}$

  

## Characteristic Equations


D:  $Q_+ = D$

J-K:  $Q_+ = J \bar{Q} + \bar{K} Q$


T:  $Q_+ = T \bar{Q} + \bar{T} Q$

E.g., J=K=0, then  $Q_+ = Q$   
 J=1, K=0, then  $Q_+ = 1$   
 J=0, K=1, then  $Q_+ = \bar{Q}$   
 J=1, K=1, then  $Q_+ = \bar{Q}$
 
## Implementing One FF in Terms of Another



D implemented with J-K

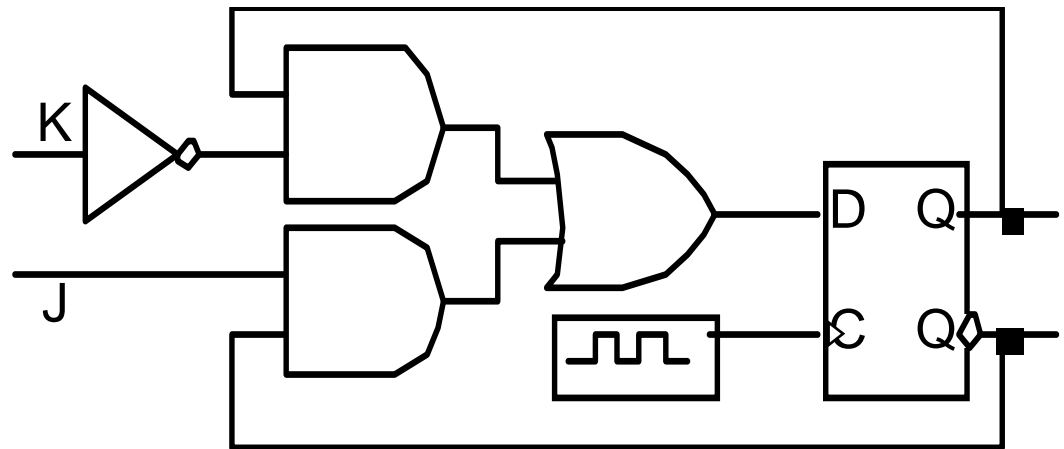


J-K implemented with D

**Excitation Tables:** What are the necessary inputs to cause a particular kind of change in state?



Q	Q+	J	K	T	D
0	0	0	X	0	0
0	1	1	X	1	1
1	0	X	1	1	0
1	1	X	0	0	1

**Implementing D FF with a J-K FF:**

 - 1) Start with K-map of  $Q^+ = f(D, Q)$
- 2) Create K-maps for J and K with same inputs (D, Q)
- 3) Fill in K-maps with appropriate values for J and K to cause the same state changes as in the original K-map



  
E.g.,  $D = Q = 0$ ,  $Q^+ = 0$   
then  $J = 0$ ,  $K = X$



Implementing J-K FF with a D FF:

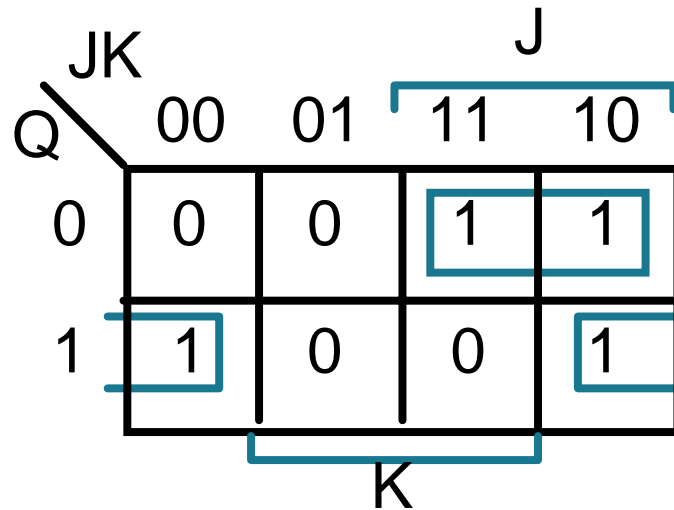
1) K-Map of  $Q^+ = F(J, K, Q)$

2,3) Revised K-map using D's excitation table  
 its the same! that is why design procedure with D FF is simple!



$$Q^+ = D = J\bar{Q} + \bar{K}Q$$

 Resulting equation is the combinational logic input to D to cause same behavior as J-K FF. Of course it is identical to the characteristic equation for a J-K FF.



## Register Timing Parameters

$T_{cq}$  : worst case rising edge  
clock to q delay

$T_{cq, cd}$  : contamination or  
minimum delay from  
clock to q


$T_{su}$  : setup time

$T_h$  : hold time

 
## Logic Timing Parameters

$T_{logic}$  : worst case delay  
through the combinational  
logic network

$T_{logic, cd}$  : contamination or  
minimum delay  
through logic network




$$T > T_{cq} + T_{logic} + T_{su}$$

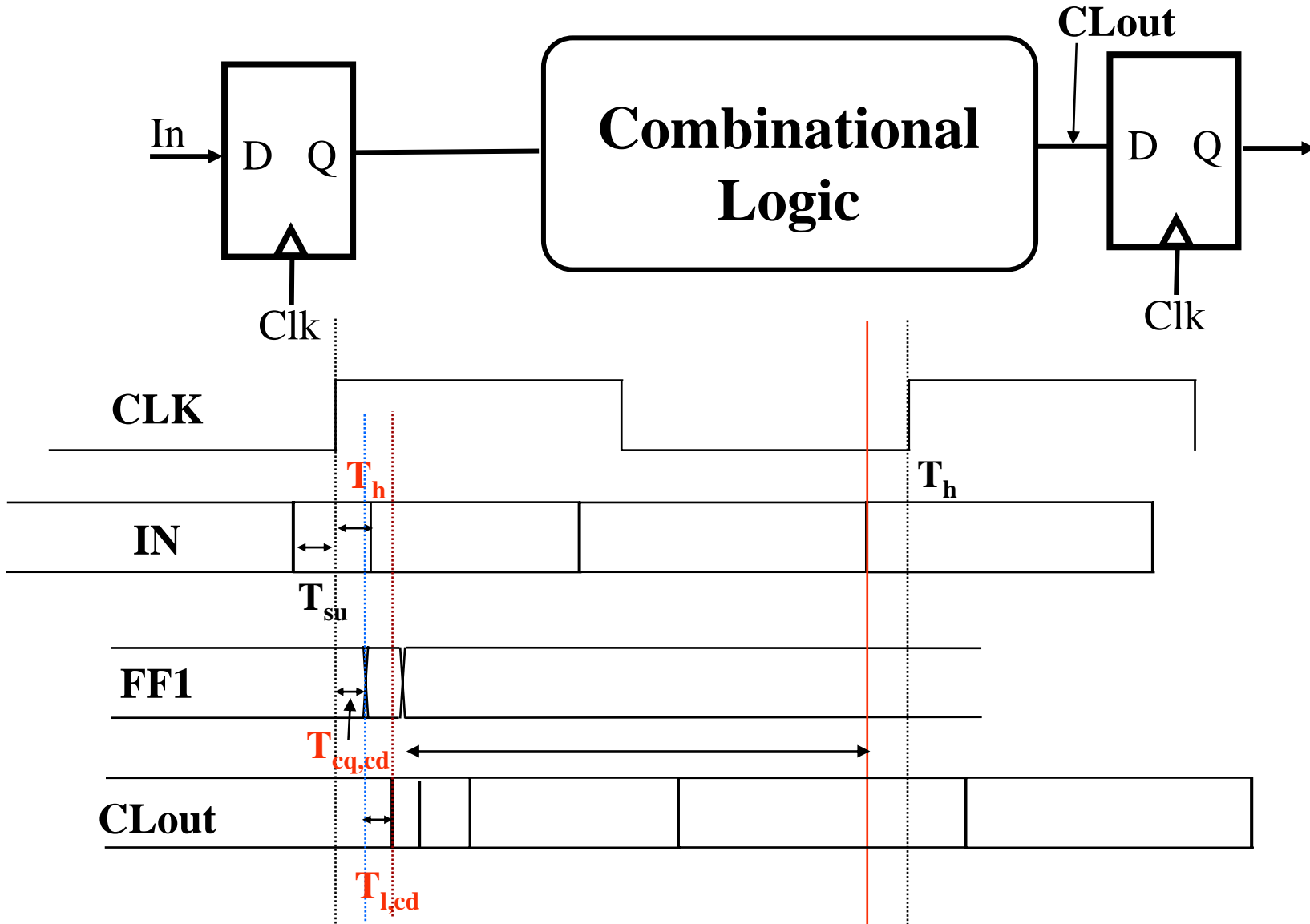

$$T_{cq,cd} + T_{logic,cd} > T_{hold}$$


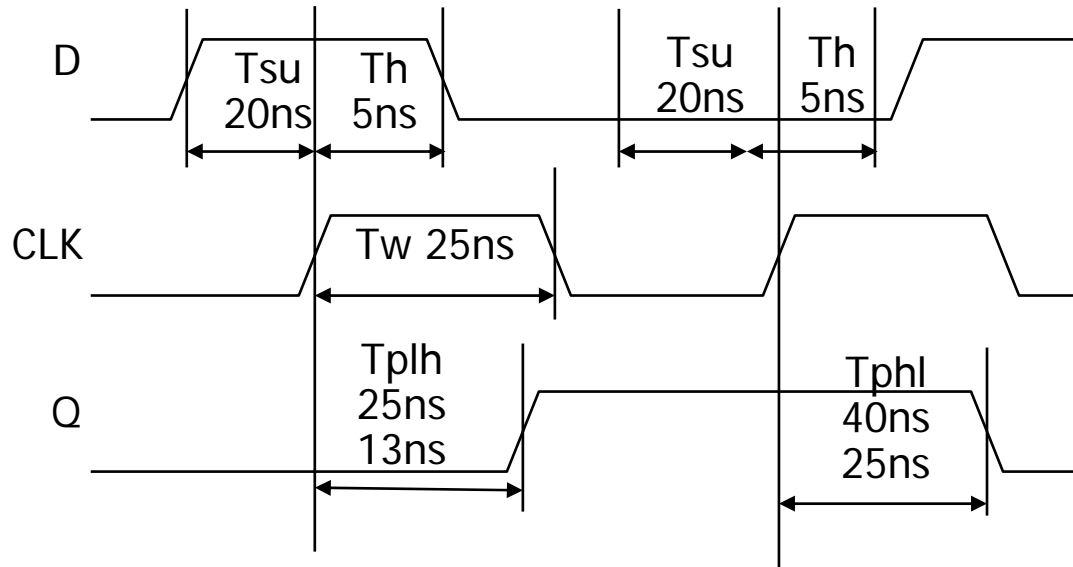
## ■ Typical parameters for Positive edge-triggered D Register



all measurements are made from the clocking event that is, the rising edge of the clock

## ■ Shift-register

