

Using State Variable Filter to Create Lead/Lag Filters

Royal Johnson

April 29, 2004

Introduction

The state variable filter serves as an example of a low-pass, high-pass and band-pass filter. The filter is unique because it is based on the idea that any transfer function can be created using only integrators and gain blocks as its basic components. This filter also serves as a starting point to creating other filters such as lead and lag filters used in compensators for control systems.

State-Variable Filter (SVF)

The state-variable filter uses two integrators and one gain block to create a filter that exhibits a low-pass, band-pass or high-pass characteristic based on where the output is realized. The basic state-variable filter is presented in Figure 1.

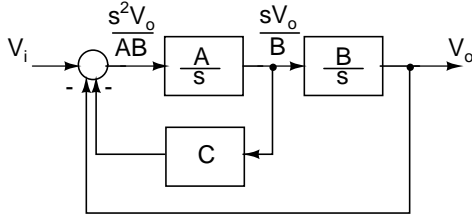


Figure 1: State-Variable Filter

The low-pass, band-pass and high-pass outputs are represented by V_o , $\frac{sV_o}{B}$ and $\frac{s^2V_o}{AB}$ respectively, which from here on in, will be referred to as V_o , V_2 and V_1 . The respective transfer functions are represented by Equations 1-3.

$$\frac{V_o}{V_i} = \frac{AB}{s^2 + CA s + AB} \quad (1)$$

$$\frac{V_o}{V_2} = \frac{sA}{s^2 + CA s + AB} \quad (2)$$

$$\frac{V_o}{V_1} = \frac{s^2}{s^2 + CA s + AB} \quad (3)$$

These three equations show that it is possible to realize transfer functions with the order of the numerator less than or equal to the order of

the denominator without the use of feed-forward zeros. In other words:

$$\Theta(Num) \leq \Theta(Den) \quad (4)$$

is possible using only integrators.

Modifying SVF for Lead/Lag Compensators

The lead compensator is a very useful filter in control theory. This filter is used to add phase margin to a system close to instability. The lead compensator transfer function is realized with one pole and one zero. The lead zero is at a lower frequency than that of its pole, creating a phase bump at a frequency equalling the geometric mean of the pole and zero. The lead transfer function is:

$$H = \frac{\tau_1 s + 1}{\tau_2 s + 1}, \tau_1 > \tau_2 \quad (5)$$

In order to realize the 'lead' transfer function, the low-pass transfer function from the SVF is analyzed. Some modifications are however necessary. First, the ' s^2 ' in the denominator needs to disappear, and secondly, there needs to be a ' s ' as the second term in the numerator. The latter can be realized by adding a feed-forward path to the SVF as shown in Figure 2.

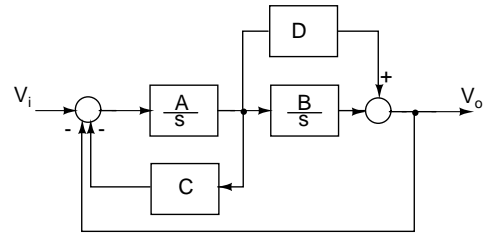


Figure 2: State-Variable Filter, Modified

The resulting transfer function of this configuration is:

$$\frac{V_o}{V_i} = \frac{A(Ds + B)}{s^2 + A(C + D)s + AB} \quad (6)$$

The next step is to now eliminate the ' s^2 ' term. It is clear that ' A ' multiplies all terms except the

$$V_2 = -\frac{i}{Cs} = -\frac{G_1(V_{in} - V_{out})}{Cs} \quad (15)$$

$$V_{out} = \frac{G_3(V_1 - V_2)}{G_3} = V_1 - V_2 \quad (16)$$

$$\tau_1 = \frac{C}{G_2} \quad (18)$$

$$\tau_2 = \frac{(G_1 + G_2)C}{G_1G_2} \quad (19)$$

After a little algebra, the transfer function is realized as:

$$\frac{V_{out}}{V_{in}} = \frac{\frac{Cs}{G_2} + 1}{\frac{(G_1 + G_2)Cs}{G_1G_2} + 1} \quad (17)$$

In this configuration, the circuit is a lag filter, because $\tau_2 > \tau_1$. To make this circuit into a lead filter, the inputs to the G_1 filter need to be switched, specifically, V_{in} connects to the negative terminal and V_{out} connects to the positive terminal. Two birds with one stone!